

# Verilog HDL

---

A Brief Introduction

Fall 2020

<https://web.cs.hacettepe.edu.tr/~bbm231/>

<https://piazza.com/hacettepe.edu.tr/fall2020/bbm231233>

# Outline


- **Introduction**
  - **Hardware Description Languages**
  - **Different Levels of Abstraction**
  - **Getting Started With Verilog**
  - **Verilog Language Features**
  - **Test benches and Simulation**
-

# Introduction

As digital and electronic circuit designs grew in size and complexity, capturing a large design at the gate level of abstraction with schematic-based design became

- **Too complex,**
- **Prone to error,**
- **Extremely time-consuming.**

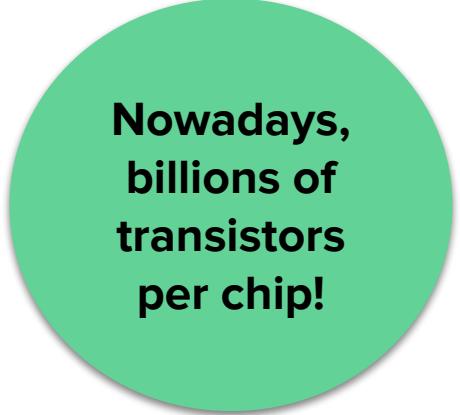Complex digital circuit designs require a lot more time for development, synthesis, simulation and debugging.



Nowadays,  
billions of  
transistors  
per chip!

Moore's Law?

## Solution? Computer Aided Design (CAD) tools

- Based on Hardware Description Languages

# Hardware Description Language (HDL)

HDLs are specialized computer languages used to program electronic and digital logic circuits.

- High level languages with which we can specify our HW to analyze its design before actual fabrication.


## Two most popular HDLs:

- Verilog
- VHDL

## Other popular HDLs:

- SystemC
- SystemVerilog
- ...

# Design Flow (Simplified)

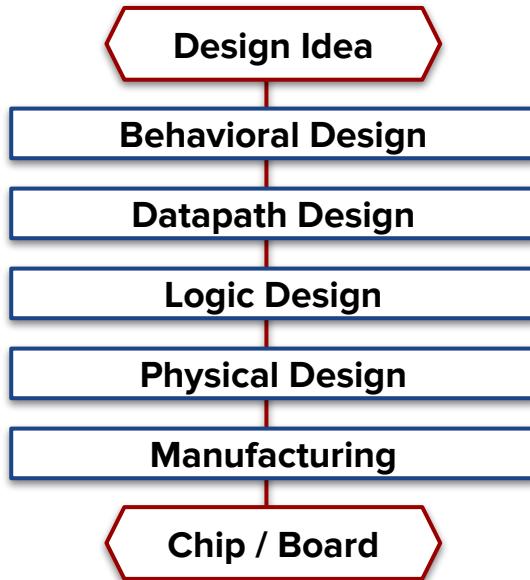


**Some other steps in design:**

- **Simulation** to verify the design (at different levels)
- **Formal verification**
- etc.

# Different Levels of Abstraction
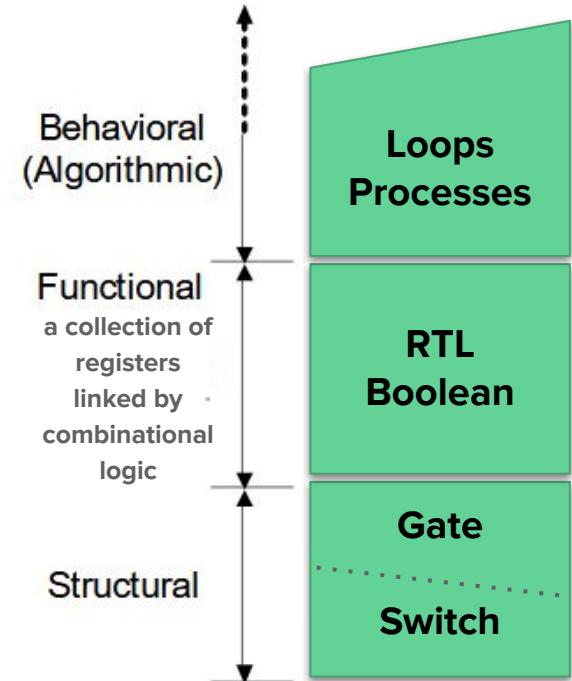
## Behavioral vs. Structural Design

- **Behavioral:** the highest level of abstraction - specifying the functionality in terms of its ***behavior*** (e.g. Boolean equations, truth tables, algorithms, code, etc.). **WHAT, not HOW.**
- **Structural:** a netlist specification of components and their interconnections (e.g. gates, transistors, even functional modules).



We will use both.

## Example: Full Adder

# Different Levels of Abstraction

- Behavioral modeling:


A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table

$$\begin{aligned} \text{Cout} &= B \text{ Cin} + A \text{ Cin} + A B \\ S &= A' B' \text{ Cin} + A' B \text{ Cin}' + A B' \text{ Cin}' + A B \text{ Cin} \\ &= A' (B' \text{ Cin} + B \text{ Cin}') + A (B' \text{ Cin}' + B \text{ Cin}) \\ &= A' Z + A Z' \\ &= A \text{ xor } Z = A \text{ xor } (B \text{ xor } \text{Cin}) \end{aligned}$$

In terms of Boolean  
expressions

- Structural modeling:

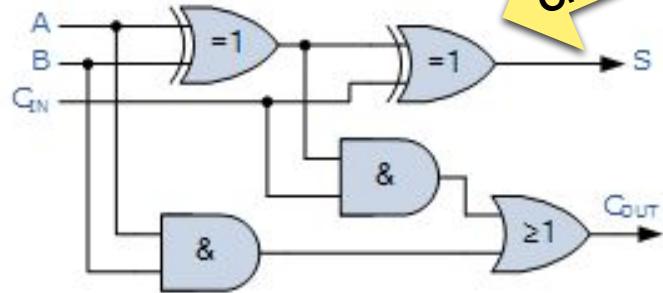



Circuit diagram

```
module full_adder(x,y,cin,s,cout);
    input x,y,cin;
    output s,cout;
    wire s1,c1,c2,c3;
    xor(s1,x,y);
    xor(s,cin,s1);
    and(c1,x,y);
    and(c2,y,cin);
    and(c3,x,cin);
    or(cout,c1,c2,c3);
endmodule
```

Verilog module with  
structural design
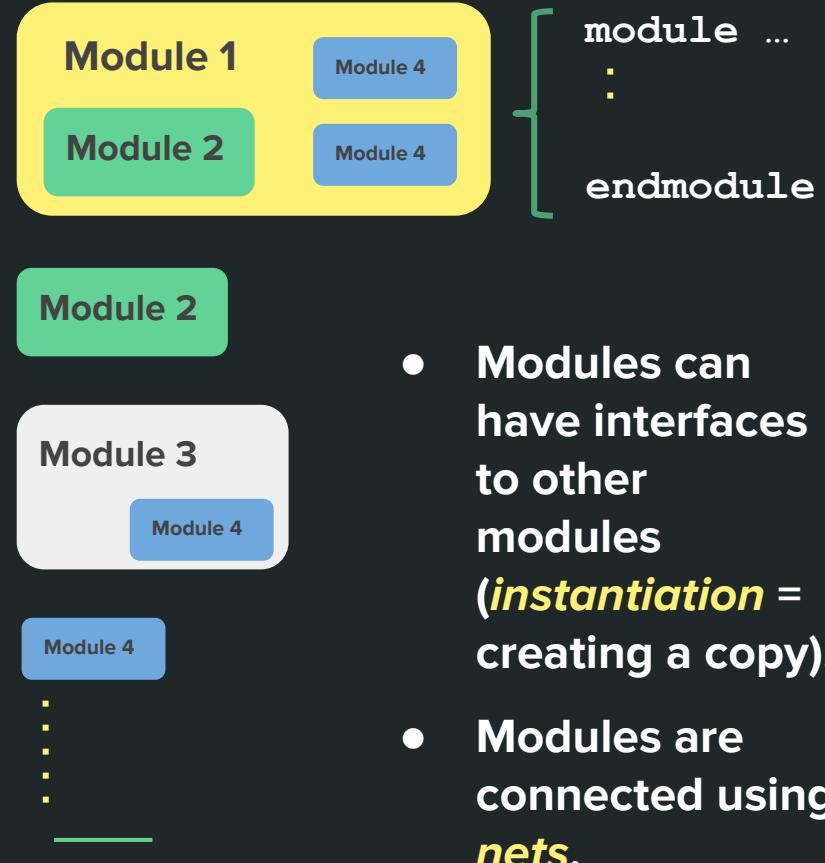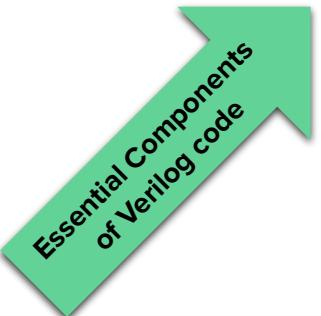
# Getting Started With Verilog

Describing a digital system as a  
set of modules





# What can we do?

- **Simulation** to verify the system (test benches)
- **Synthesis** to map to hardware (low-level primitives, ASIC, FPGA)



We'll be doing this.

# Development Process

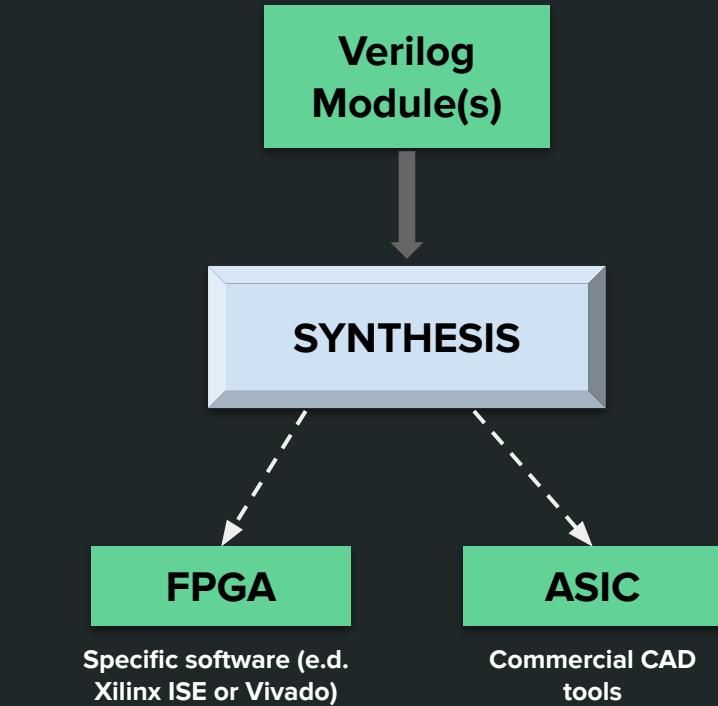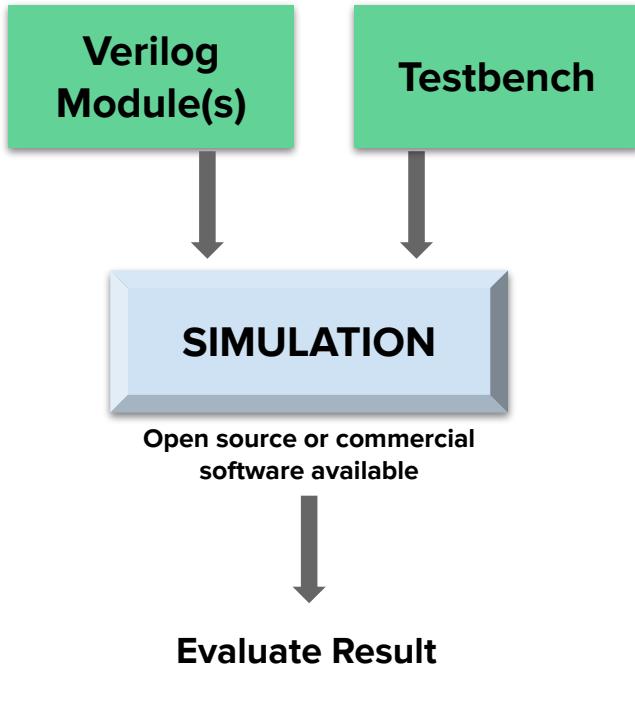

# Verilog Language Features

## Operators

### Arithmetic Operators:

+	unary (sign) plus
-	unary (sign) minus
+	binary plus (add)
-	binary minus (subtract)
*	multiply
/	divide
%	modulus
**	exponentiation

### Examples:

– (b + c)  
(a – b) + (c \* d)  
(a + b) / (a – b)  
a % b  
a \*\* 3

# Verilog Language Features

## Operators

### Logical Operators:

!	logical negation
&&	logical AND
	logical OR

E&F

A	B	A && B
F	F	F
F	T	F
T	F	F
T	T	T

### Examples:

(done && ack)  
(a || b)  
!(a && b)  
((a > b) || (c ==0))  
((a > b) && !(b > c))

Evaluates to True or False

# Verilog Language Features

## Operators

### Relational Operators:

<code>!=</code>	not equal
<code>==</code>	equal
<code>&gt;=</code>	greater or equal
<code>&lt;=</code>	less or equal
<code>&gt;</code>	greater
<code>&lt;</code>	less

### Examples:

(`a != b`)  
(`((a + b) == (c - d))`)  
(`((a > b) && (c < d))`)  
(`count <= 0`)

Operate on numbers,  
return True or False

# Verilog Language Features

## Operators

### Bitwise Operators:

<code>~</code>	bitwise NOT
<code>&amp;</code>	bitwise AND
<code> </code>	bitwise OR
<code>^</code>	bitwise exclusive-OR
<code>~^</code>	bitwise exclusive-NOR

### Examples:

```
wire a, b, c, d, f1, f2, f3, f4;  
assign f1 = ~a | b;  
assign f2 = (a & b) | (b & c) | (c & a);  
assign f3 = a ^ b ^ c;  
assign f4 = (a & ~b) | (b & c & ~d);
```



Operate on bits, return a value that is also a bit.

# Verilog Language Features

## Operators

### Shift Operators:

**>>** shift right

**<<** shift left

**>>>** arithmetic shift right


### Examples:

```
wire [15:0] data, target;
```

```
assign target = data >> 3;
```

```
assign target = data >>> 2;
```

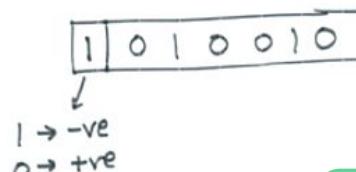$0 \rightarrow$               $\ggg ::$  2's complement number system  
 $\gg$                    $\ll$



Shift right:  $\% 2$   
Shift left :  $* 2$

Reduction, conditional,  
concatenation, and replication  
operators also available.




# Verilog Language Features

## Data Values

Verilog supports 4 value levels:

Value Level	Represents
0	Logic 0 state
1	Logic 1 state
x	Unknown logic state
z	High impedance state

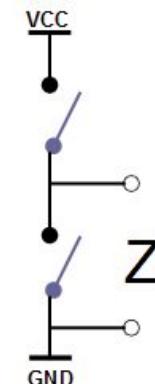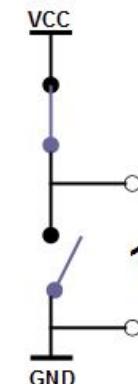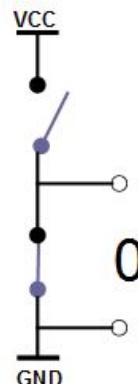- All unconnected nets are set to 'z'.
- All register variables are set to 'x'.



# Verilog Language Features

## Module - the basic unit of hardware in Verilog

- Cannot contain definitions of other modules,
- Can be *instantiated* within another module - **hierarchy of modules**.



Different than calling a function  
in programming lang.  
Every instantiation  
adds to  
area!

```
module module_name (list_of_ports);  
    input/output declarations  
    Local net declarations Temporary connections (wires)  
    Parallel statements  
endmodule
```

Why parallel?


# Verilog Language Features

## Module example: A simple AND function

```
// A simple AND function
module simple_AND(t1, a, b);
    input a, b;
    output t1;
    assign t1 = a & b;
endmodule
```

Is this a structural or behavioral description?

assign t1 = a & b;

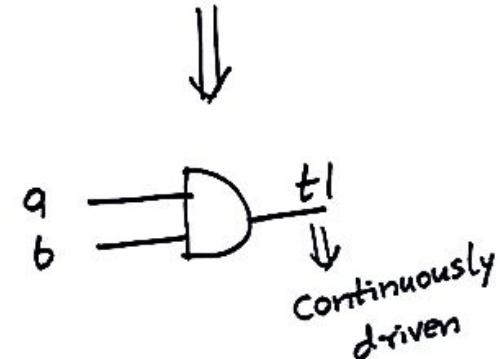

## Assign statement:

**assign var = expression;**

- used **typically** for combinational circuits.
- continuous assignment
- LHS must be “net” type var (usually “wire”)
- RHS can be both “register” or “net” type


Not synced  
with clock!

# Verilog Language Features

## Module example 2: A 2-level combinational circuit

```
// A 2-level combinational circuit
module two_level(a, b, c, d, f);
    input a, b, c, d;
    output f;
    wire t1, t2; // intermediate lines
    assign t1 = a & b;
    assign t2 = ~(c | d);
    assign f = ~(t1 & t2);
endmodule
```

This is also a behavioral description.

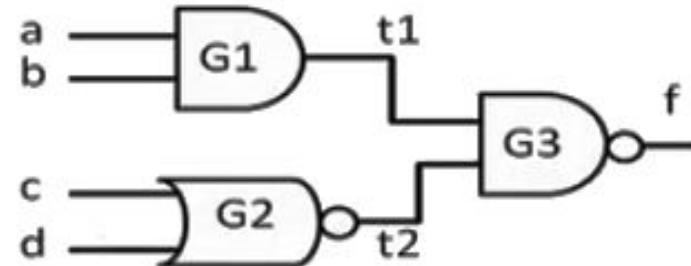

# Verilog Language Features

## Data Types

A variable can be:


A. Net **wire, wor, wand, tri, supply0, supply1, etc.**

- Must be continuously driven,
- Cannot be used to store a value,
- Models connections between continuous assignments and instantiations,
- 1-bit values by default, unless declared as vectors explicitly.
- Default value of a *net* is “Z” - high impedance state.

B. Register **reg, integer, real, time**

- Retains the last value assigned to it,
- Usually used to represent storage elements (sometimes in combinational circuits),
- May or may not map to a HW register during synthesis.
- Default value of a *reg* data type is “X”.

```
wire sbar;  
assign sbar = ~S;
```

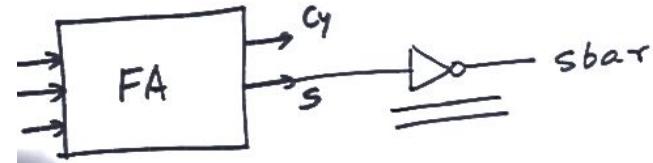


# Verilog Language Features

## Data Types

net example:

```
module use_wire(a, b, c, d, f);
    input a, b, c, d;
    output f;
    wire f; // net f declared as wire
    assign f = a & b;
    assign f = c | d;
endmodule
```

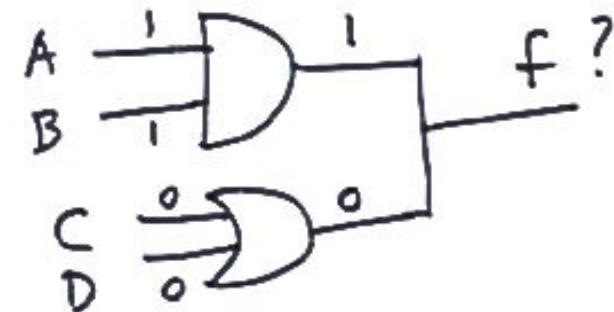

Is this a valid design?


# Verilog Language Features

## Data Types

net example:

```
module use_wire(a, b, c, d, f);
    input a, b, c, d;
    output f;
    wire f; // net f declared as wire
    assign f = a & b;
    assign f = c | d;
endmodule
```

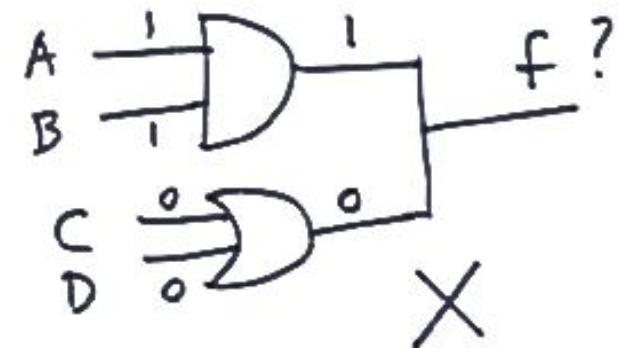For these inputs, f will  
be indeterminate!




Wrong design!

# Verilog Language Features

## Data Types

net example - correct design:

```
// A 2-level combinational circuit
module using_wand(a, b, c, d, f);
    input a, b, c, d;
    output f;
    wand f; // net f declared as wand
    assign f = a & b;
    assign f = c | d;
endmodule
```

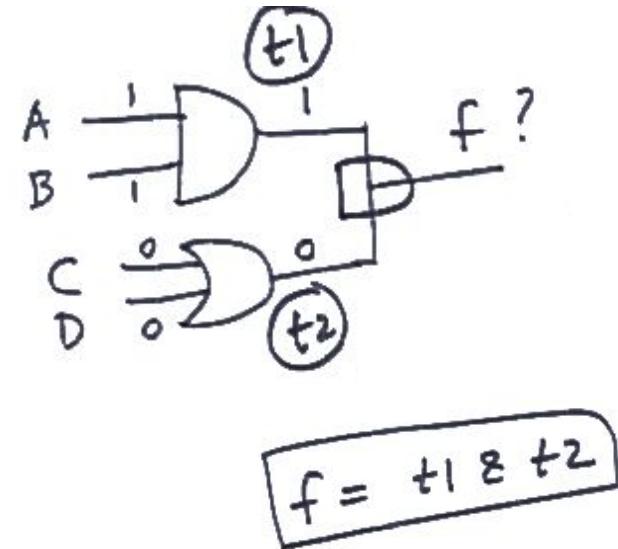

Here, function realized will be  
 $f = (A \& B) \& (C | D)$

# Verilog Language Features

## Data Types

### net example 2:

```
module using_supply_wire(a, b, c, f);
    input a, b, c;
    output f;
    wire t1, t2;
    supply0 gnd;
    supply1 vcc;
    nand G1 (t1, vcc, a, b);
    xor G2 (t2, c, gnd);
    and G3 (f, t1, t2);
endmodule
```

Is this a structural or behavioral description?

# Verilog Language Features

## Data Types

### reg example:

- Declaration explicitly specifies the size (default is 1-bit):
  - `reg x, y; // 1-bit register variables`
  - `reg [7:0] bus; // An 8-bit bus`
- Treated as an unsigned number in arithmetic expressions.
- **MUST** be used when modeling actual ***sequential*** HW, e.g. counters, shift registers, etc.
- Two types of assignments possible:
  - `A = B + C;`
  - `A <= B + C;`



For 2's comp. signed  
use integer data type

A must be a  
reg type var

# Verilog Language Features

## Data Types


**reg example - 32-bit counter with synchronous reset:**

```
module simple_counter(clk, rst, count);
    input clk, rst;
    output [31:0] count;
    reg [31:0] count;

    always @(posedge clk)
    begin
        if(rst)
            count = 32'b0;
        else
            count = count + 1;
    end
endmodule
```

Because we must have  
a **reg** type var at LHS  
Otherwise: compiler error

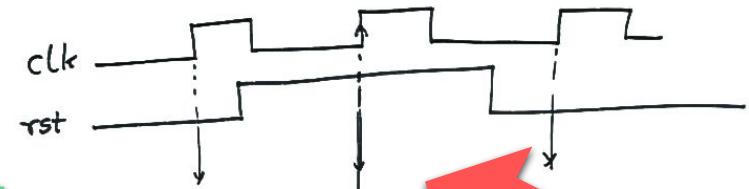If **rst** is high, reset  
occurs at the positive  
edge of the next clock.



How to fix this?

Any variable assigned  
within the *always* block  
must be of type **reg**.

# Verilog Language Features

## Data Types

**reg example - solution: 32-bit counter with asynchronous reset:**

```
module simple_counter(clk, rst, count);
    input clk, rst;
    output [31:0] count;
    reg [31:0] count;

    always @(posedge clk or posedge rst)
    begin
        if(rst)
            count = 32'b0;
        else
            count = count + 1;
    end
endmodule
```

Reset occurs whenever  
rst goes high.

# Verilog Language Features

## Data Types

### Integer example:

- General purpose register data type,
- 2's complement signed integer in arithmetic expressions,
- Default size is 32 bits.

```
wire [15:0] X, Y;  
integer C;
```

```
C = X + Y;
```

In Verilog, when you perform arithmetic operations, such as addition, on vectors (like [15:0] X and [15:0] Y in your code), the result is automatically extended to accommodate any possible overflow or carry-out from the most significant bit. This means that if the sum of X and Y results in a carry-out from the most significant bit (bit 15 in this case), the result will be 17 bits wide to include the carry.

Synthesis tool deduces that  
C is 17 bits (16 bits + a carry)


Other register  
data types:  
*real, time.*

# Verilog Language Features
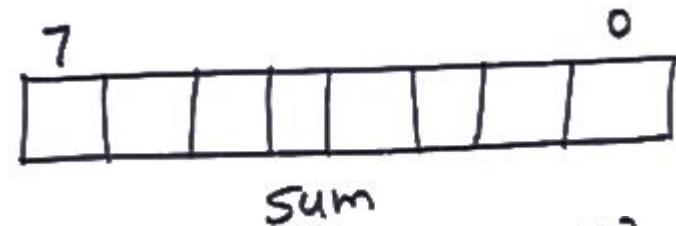
## Vectors

- Both **Net** or **reg** type variables can be declared as vectors: **multiple bit widths**
- Specifying width with: **[MSB:LSB]**

```
wire x, y, z;      // single bit variables  
wire[7:0] sum;    // MSB is sum[7], LSB is sum[0]  
reg [1:10] data;  // MSB is data[1], LSB is data[10]  
reg clock;
```



sum[0]  
sum[1]  
;  
sum[7]


# Verilog Language Features

## Vectors

- Parts of a vector can be addressed and used in an expression:

```
reg [31:0] IR;           opcode = IR[31:26];  
reg [5:0] opcode;        reg1 = IR[25:21];  
reg [4:0] reg1, reg2, reg3; reg2 = IR[20:16];  
reg [10:0] offset;       reg3 = IR[15:11];  
                         offset = IR[10:0];
```

$$SUM = IR[25:21] + IR[20:16]$$

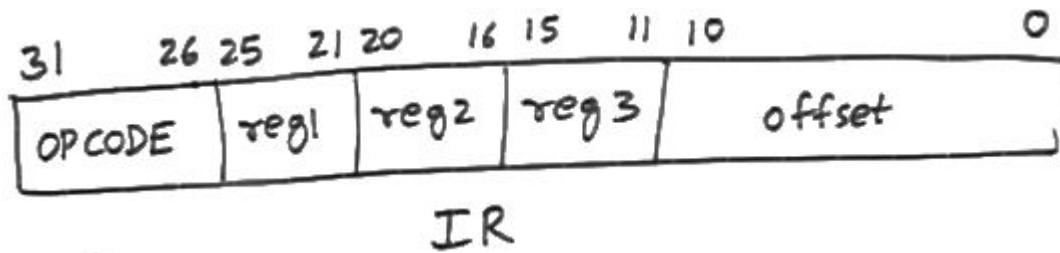

Multi-dimensional arrays and memories also possible.

# Verilog Language Features

## Constant Values

- Sized or unsized form,
- Syntax:
  - `<size>'<base><number>`
- Examples:

`4'b0101`

`// 4-bit binary number 0101`

`1'b0`

`// Logic 0 (1-bit)`

`B`

`3`

`C`

`12'hB3C`

`// 12-bit number 1011 0011 1100`

`12'h8xF`

`// 12-bit number 1000 xxxx 1111`

`25 h = hexaDecimal`

`// signed number, in 32 bits (size not specified)`

# Verilog Language Features

## Parameters

- Constants with a given name,
- Size deduced from the constant value itself:

```
parameter HI = 5, LO = 0;  
parameter up = 2'b00, down = 2'b01, steady = 2'b10;
```

```
// Parameterized design:  
// an N-bit counter  
module counter(clk, rst, count);  
    parameter N = 31;  
    input clk, rst;  
    output [0:N] count;  
    reg [0:N] count;  
  
    always @(negedge clk)  
    begin  
        if (rst)  
            count = 0;  
        else  
            count = count + 1;  
    end  
endmodule
```

# Verilog Language Features

## Predefined Logic Gates

- Can be instantiated within a module to create a structural design.

### 2-input AND

$$0 \& 0 = 0$$

$$0 \& 1 = 0$$

$$1 \& 1 = 1$$

$$1 \& x = x$$

$$0 \& x = 0$$

$$1 \& z = x$$

$$z \& x = x$$

### 2-input OR

$$0 | 0 = 0$$

$$0 | 1 = 1$$

$$1 | 1 = 1$$

$$1 | x = 1$$

$$0 | x = x$$

$$1 | z = x$$

$$z | x = x$$

### 2-input EXOR

$$0 ^ 0 = 0$$

$$0 ^ 1 = 1$$

$$1 ^ 1 = 0$$

$$1 ^ x = x$$

$$0 ^ x = x$$

$$1 ^ z = x$$

$$z ^ x = x$$



Remember that Verilog  
supports 4 value levels.

There are also other gates with tristate control

# Verilog Language Features

## List of Some Primitive Gates

```
and Gate1 (out, in1, in2);  
nand Gate2 (out, in1, in2);  
or Gate3 (out, in1, in2);  
nor Gate4 (out, in1, in2);  
xor Gate5 (out, in1, in2);  
xnor Gate6 (out, in1, in2);  
not Gate7 (out, in1);
```




Number of inputs  
can be arbitrary.

and G (a, b, c, d, e, f);

output

inputs

A 5-input AND gate

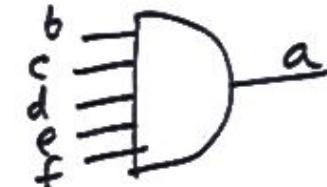


In Verilog, the term "net" refers to a data signal or a wire that carries information within a digital design.

- Output ports must be connected to a net
- Input ports may be either net or reg type vars

just remember reg is different from a net

# Verilog Language Features
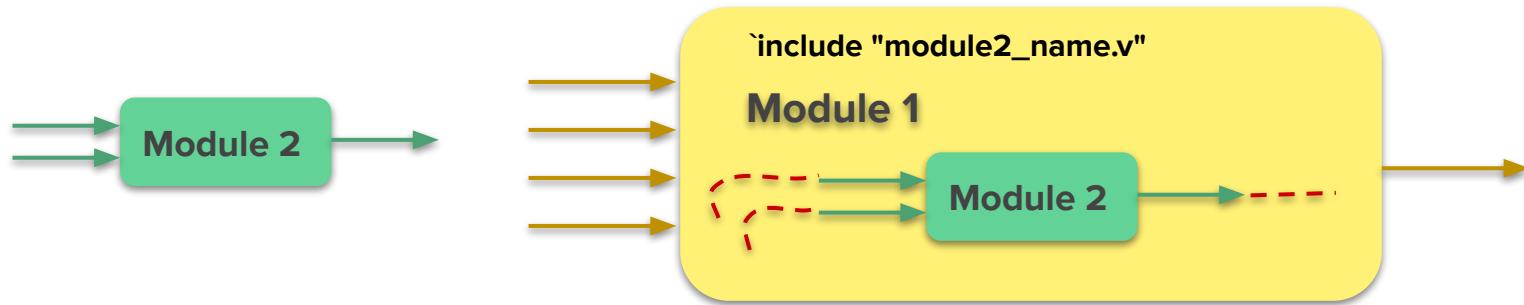
## Two Ways to Specify Connectivity During Module Instantiation






- **Positional Association (Implicit)**
  - Parameters listed in the same order as in the original module description.
- **Explicit Association**
  - Parameters explicitly listed in arbitrary order.

# Verilog Language Features

- Positional Association Example - Full Adder Using Half Adder Module




A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

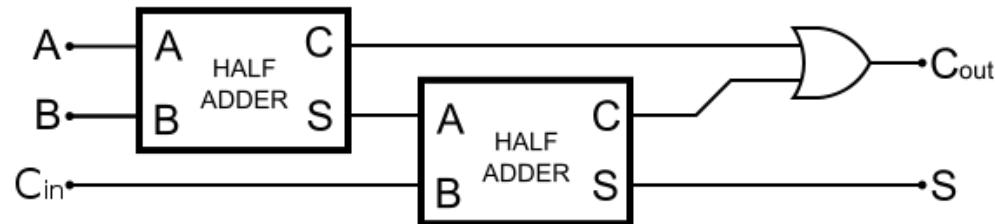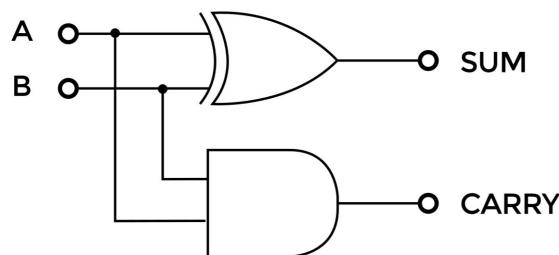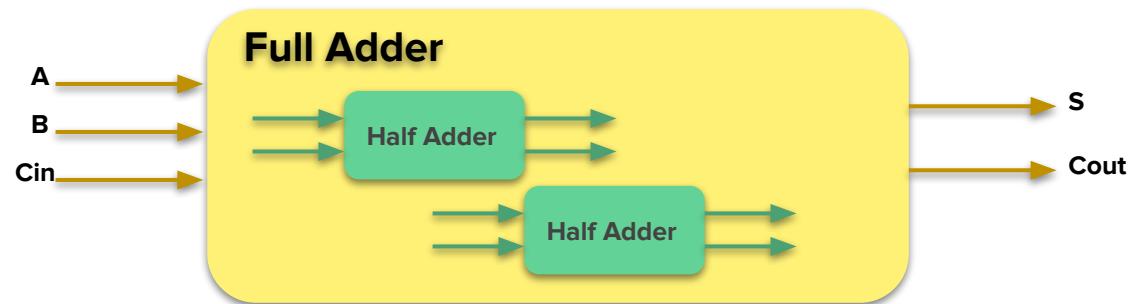
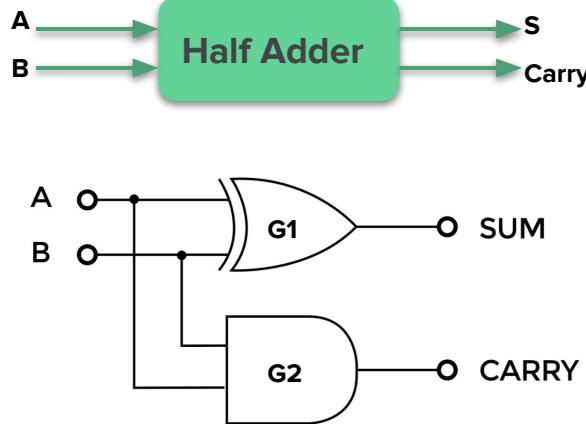
# Verilog Language Features

- Positional Association Example - Full Adder Using Half Adder Module




```
module half_adder (Sum, Carry, A, B);
    input A, B;
    output Carry, Sum;
    //structural description
    xor G1(Sum, A, B);
    and G2(Carry, A, B);
endmodule
```

What is the equivalent behavioral design?
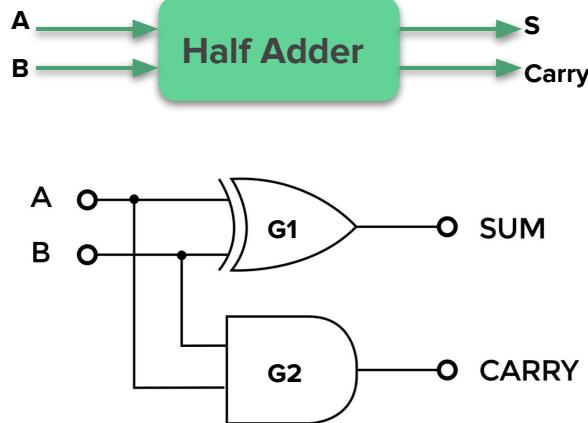
# Verilog Language Features

- Positional Association Example - Full Adder Using Half Adder Module





```
module half_adder (Sum, Carry, A, B);
    input A, B;
    output Carry, Sum;
    //structural description
    xor G1(Sum, A, B);
    and G2(Carry, A, B);
endmodule
```

```
//behavioral description
assign Sum = A ^ B;
assign Carry = A & B;
```
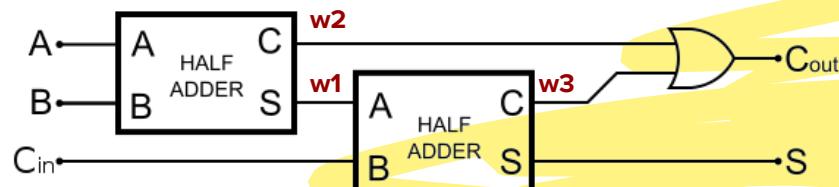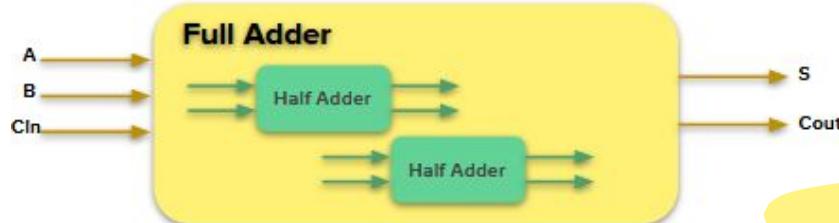
# Verilog Language Features

Note the port order

- Positional Association Example - Full Adder Using Half Adder Module



```
module half_adder (Sum, Carry, A, B);
```

```
module full_adder (Sum, Cout, A, B, Cin);
    input A, B, Cin;
    output Cout, Sum;
    wire w1, w2, w3;
```



How do we use the half\_adder module to implement a full adder?

```
endmodule
```
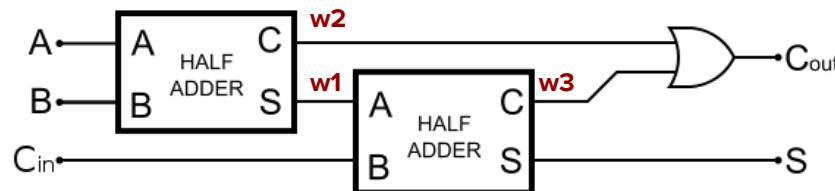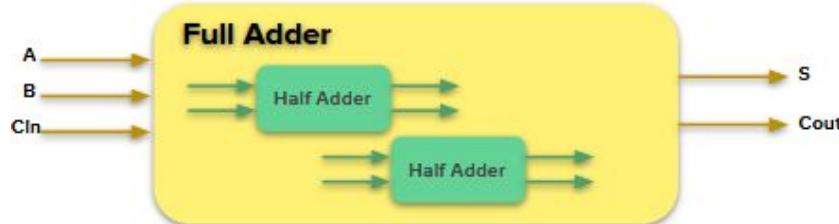
# Verilog Language Features

Note the port order

- Positional Association Example - Full Adder Using Half Adder Module




```
module half_adder (Sum, Carry, A, B);
```

```
module full_adder (Sum, Cout, A, B, Cin);
    input A, B, Cin;
    output Cout, Sum;
    wire w1, w2, w3;
    half_adder HA1 (w1, w2, A, B);
    half_adder HA2 (Sum, w3, Cin, w1);
    or (Cout, w2, w3);
endmodule
```
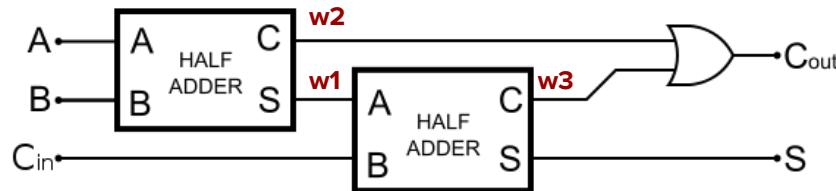
# Verilog Language Features

- Explicit Association Example - Full Adder Using Half Adder Module



```
module half_adder (Sum, Carry, A, B);
```

```
module full_adder (Sum, Cout, A, B, Cin);
    input A, B, Cin;
    output Cout, Sum;
    wire w1, w2, w3;
    half_adder HA1 (.A(A), .B(B), .Sum(w1), .Carry(w2));
    half_adder HA2 (.Sum(Sum), .Carry(w3), .B(Cin), .A(w1));
    or (Cout, w2, w3);
endmodule
```

Ports are explicitly specified - order is not important

Less chance for errors


# Verilog Language Features
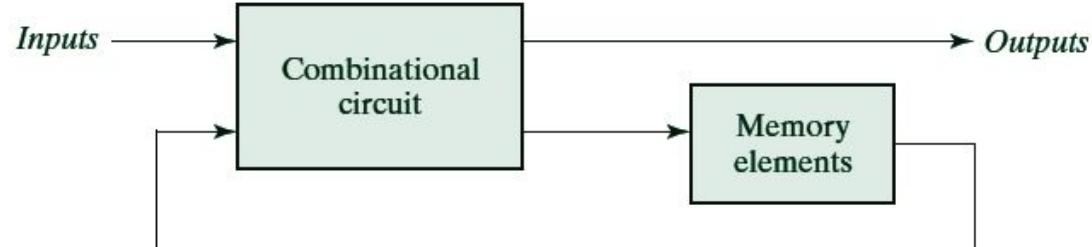
## Combinational vs. Sequential Circuits

**Combinational:** The output only depends on the present input.



**Sequential:** The output depends on both the present input and the previous output(s) (the state of the circuit).



# Verilog Language Features

## Combinational vs. Sequential Circuits

**Sequential logic:** Blocks that have memory elements: Flip-Flops, Latches, Finite State Machines.

- Triggered by a ‘clock’ event.
  - Latches are sensitive to level of the signal.
  - Flip-flops are sensitive to the transitioning of clock

Combinational constructs are not sufficient. We need new constructs:

- **always**
- **initial**

**always @ (sensitivity list)  
statement;**

# Verilog Language Features

## Sequential Circuits

```
always @ (sensitivity list)  
statement;
```

Whenever the event in the sensitivity list occurs, the statement is executed.



Remember our  
counter example

```
module simple_counter(clk, rst, count);  
    input clk, rst;  
    output [31:0] count;  
    reg [31:0] count;  
  
    always @(posedge clk)  
    begin  
        if(rst)  
            count = 32'b0;  
        else  
            count = count + 1;  
    end  
endmodule
```

# Verilog Language Features

## Sequential Circuits

- Sequential statements are within an '**always**' block,
- The sequential block is triggered with a change in the sensitivity list,
- Signals assigned within an **always** block must be declared as **reg**,
  - The values are preserved (memorized) when no change in the sensitivity list.
- We do not use '**assign**' within the **always** block.

### ■ Always blocks allow powerful statements

- **if .. then .. else**
- **case**

# Difference between Synchronous and Asynchronous Sequential Circuits

SYNCHRONOUS CIRCUIT	ASYNCHRONOUS CIRCUIT
All the <b>State Variable</b> changes are synchronized with a universal clock signal.	The <b>State Variables</b> are not synchronized to change simultaneously and may change at anytime irrespective of each other to achieve the next <b>Steady Internal State</b>
Since all the Internal State changes are in the strict control of a master clock source they are less prone to failure or to a race condition and hence are more reliable.	Since there is no such universal clock source, the internal state changes as soon as any of the inputs change and hence are more prone to a race condition.
Timings of the internal state changes are in our control.	The changes in the internal state of an asynchronous circuit are not in our control.

# Verilog Language Features

## Sequential Circuits


### 32-bit counter with synchronous reset:

```
module simple_counter(clk, rst, count);
    input clk, rst;
    output [31:0] count;
    reg [31:0] count;

    always @(posedge clk)
    begin
        if(rst)
            count = 32'b0;
        else
            count = count + 1;
    end
endmodule
```

Because we must have  
a **reg** type var at LHS  
Otherwise: compiler error

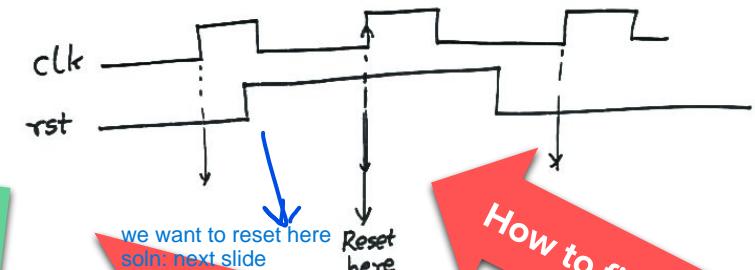If **rst** is high, reset  
occurs at the positive  
edge of the next clock.



Any variable assigned  
within the *always* block  
must be of type **reg**.

# Verilog Language Features

## Sequential Circuits

Solution: 32-bit counter with asynchronous reset:

```
module simple_counter(clk, rst, count);
    input clk, rst;
    output [31:0] count;
    reg [31:0] count;

    always @(posedge clk or posedge rst)
    begin
        if(rst)
            count = 32'b0;
        else
            count = count + 1;
    end
endmodule
```



Reset occurs whenever  
rst goes high.

# Non-blocking and Blocking Statements

## Non-blocking

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
// all assignments are made here
// b is not (yet) 2'b01
end
```

## Blocking

```
always @ (a)
begin
    a = 2'b01;
// a is 2'b01
    b = a;
// b is now 2'b01 as well
end
```

- Values are assigned at the end of the block.
- All assignments are made in parallel, process flow is not-blocked.
- Value is assigned immediately.
- Process waits until the first assignment is complete, it blocks progress.


Blocking statements allow sequential descriptions

# How to Simulate Verilog Module(s)


**Testbench:** provides stimulus to Unit-Under-Test (UUT) to verify its functionality, captures and analyzes the outputs.
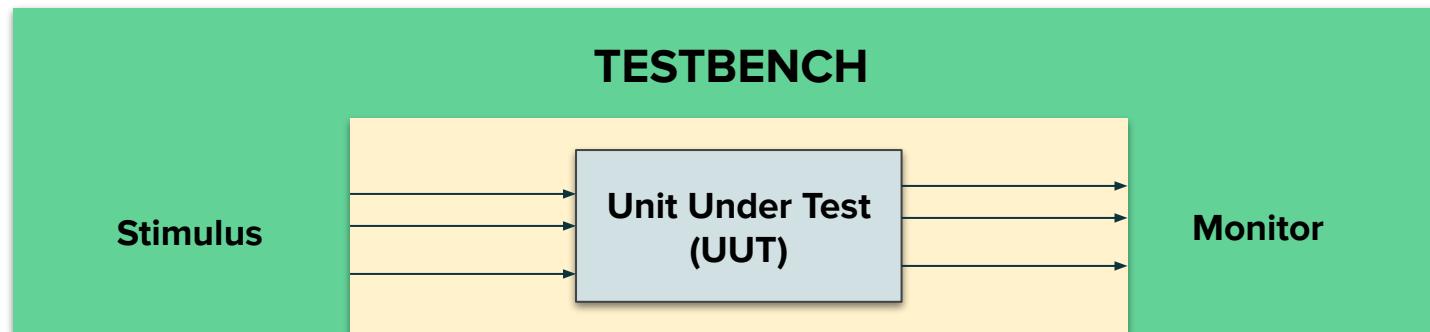
## Requirements:

Inputs and outputs need to be connected to the test bench



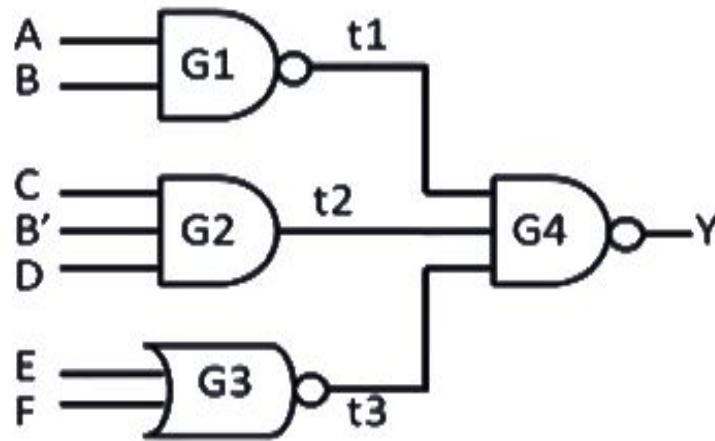
# How to Simulate Verilog Module(s) Example



Suppose we want to design  
and simulate this circuit.

We can choose  
either *behavioral*  
or *structural*  
design.
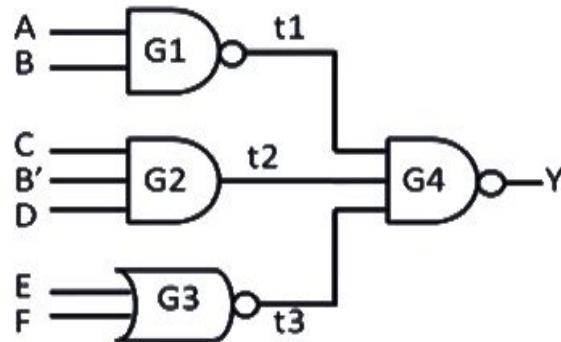
# How to Simulate Verilog Module(s) Example




Let's choose structural design:

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
```

Which gates do we need, and what will  
the connections be?

```
endmodule
```
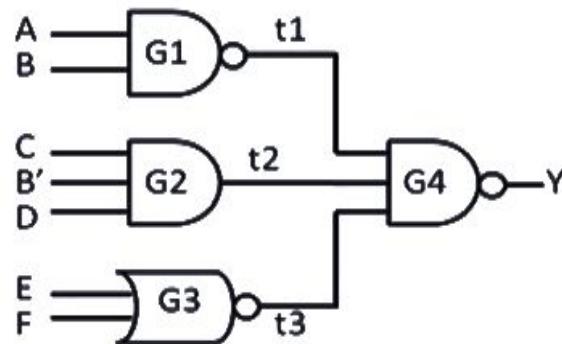
# How to Simulate Verilog Module(s) Example




Let's choose structural design:

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);

    endmodule
```
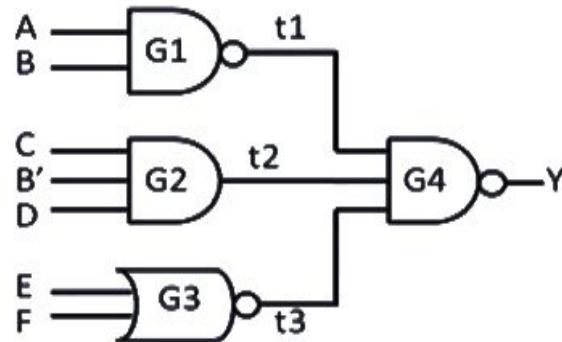
# How to Simulate Verilog Module(s) Example




Let's choose structural design:

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);

    endmodule
```
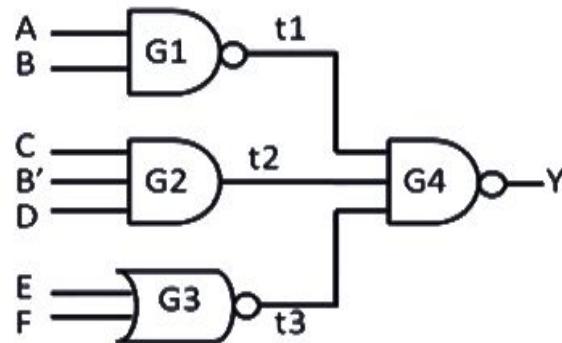
# How to Simulate Verilog Module(s) Example




Let's choose structural design:

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);

endmodule
```
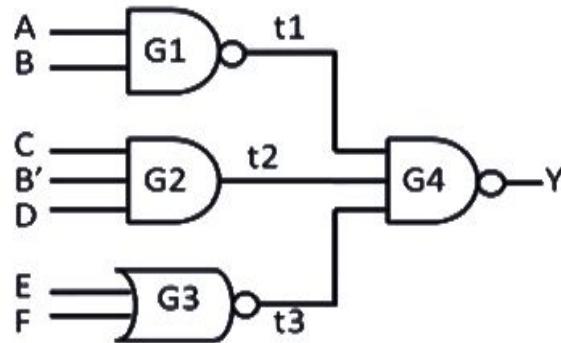
# How to Simulate Verilog Module(s) Example



Now we need to provide stimulus and monitor the outputs - TESTBENCH


Let's choose structural design:

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

# How to Simulate Verilog Module(s) Example

Saved as  
function\_Y\_testbench.v

TESTBENCH

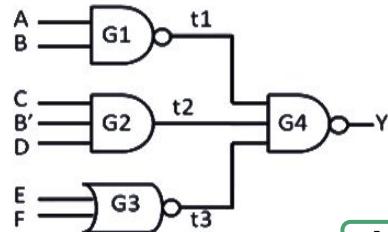

Saved as  
function\_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
endmodule
```


```
`include "function_Y.v"
module function_Y_testbench;
```

Include the module  
to be tested.

Saved as  
function\_Y\_testbench.v

# How to Simulate Verilog Module(s) Example

## TESTBENCH

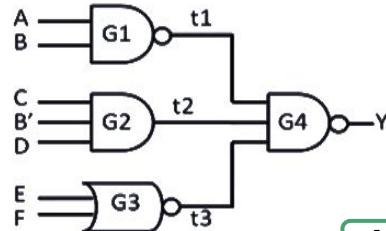

Saved as  
function\_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
endmodule
```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;
```


all input variables MUST be declared as reg, and output variables must be wire.

Vars MUST be  
declared as reg  
Output as wire

# How to Simulate Verilog Module(s) Example

Saved as  
function\_Y\_testbench.v

TESTBENCH

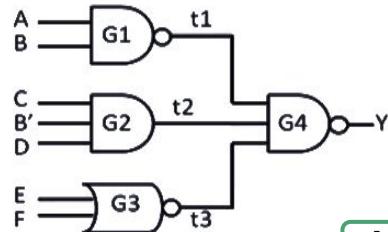

Saved as  
function\_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
endmodule
```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;


    function_Y UUT(A, B, C, D, E, F, Y);
```

Initialize Unit  
Under Test (UUT)

# How to Simulate Verilog Module(s) Example

**Saved as**  
**function\_Y\_tb.v**

## TESTBENCH

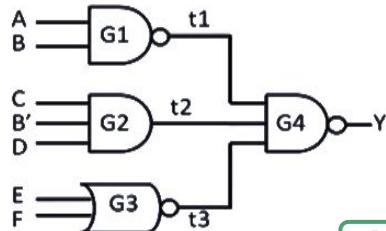

Saved as  
function\_Y.v

# Unit Under Test

```

module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule

```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;


    function_Y UUT(A, B, C, D, E, F, Y);
        initial
            begin
                |
                |
                |
            end
    endmodule
```

initial block - gets executed once

# How to Simulate Verilog Module(s) Example

Saved as  
function\_Y\_testbench.v

TESTBENCH

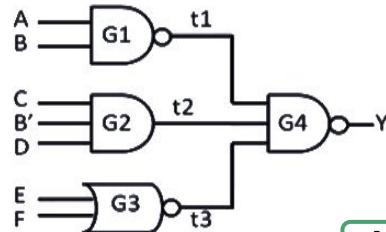

Saved as  
function\_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;

    function_Y UUT(A, B, C, D, E, F, Y);

    initial
        begin
            #10 A = 0; B = 0; C = 0; D = 0; E = 0; F = 0;
            #10 A = 1; B = 0; C = 1; D = 1; E = 0; F = 0;
            #10 A = 0; B = 1;
            #10 F = 1;
            #10 $finish;
        end
    endmodule
```

Stimulus

# How to Simulate Verilog Module(s) Example

Results can be viewed as waveforms:



# How to Simulate Verilog Module(s) Example


We can also monitor the changes and print them to the console using `$monitor`:

```
initial
begin
$monitor ($time, "A = %b, B = %b, C = %b, D = %b, E = %b, F = %b, Y = %b", A, B, C, D, E, F, Y);
#10 A = 0; B = 0; C = 0; D = 0;
#10 A = 1; B = 0; C = 1; D = 1;
#10 A = 0; B = 1;
#10 F = 1;
#10 $finish;
end
```

Tcl Console x Messages Log ? \_ □
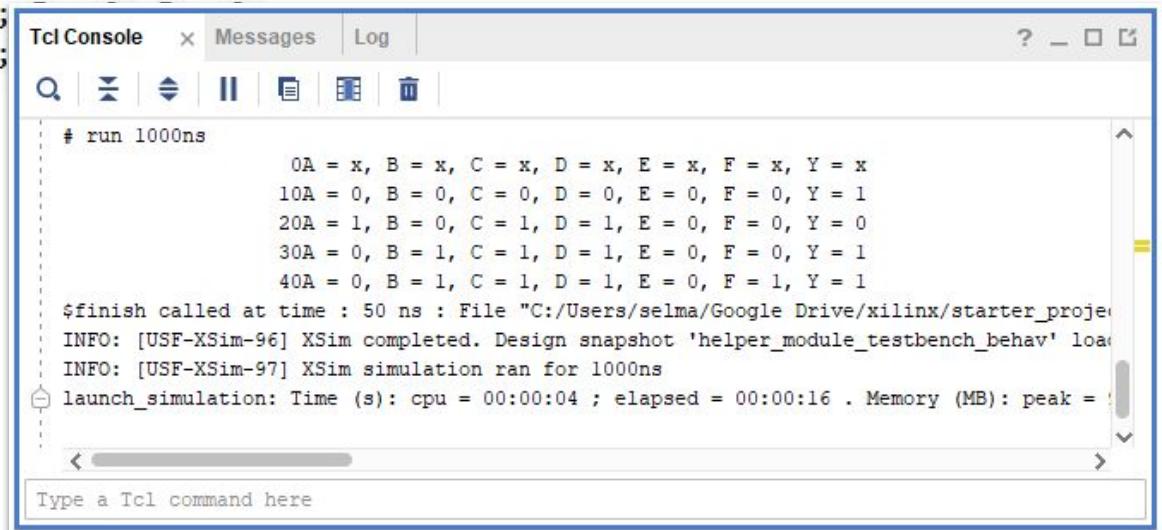
# run 1000ns


0A = x, B = x, C = x, D = x, E = x, F = x, Y = x  
10A = 0, B = 0, C = 0, D = 0, E = 0, F = 0, Y = 1  
20A = 1, B = 0, C = 1, D = 1, E = 0, F = 0, Y = 0



We can also use  
**\$dumpfile** to  
dump variable  
changes to a file.

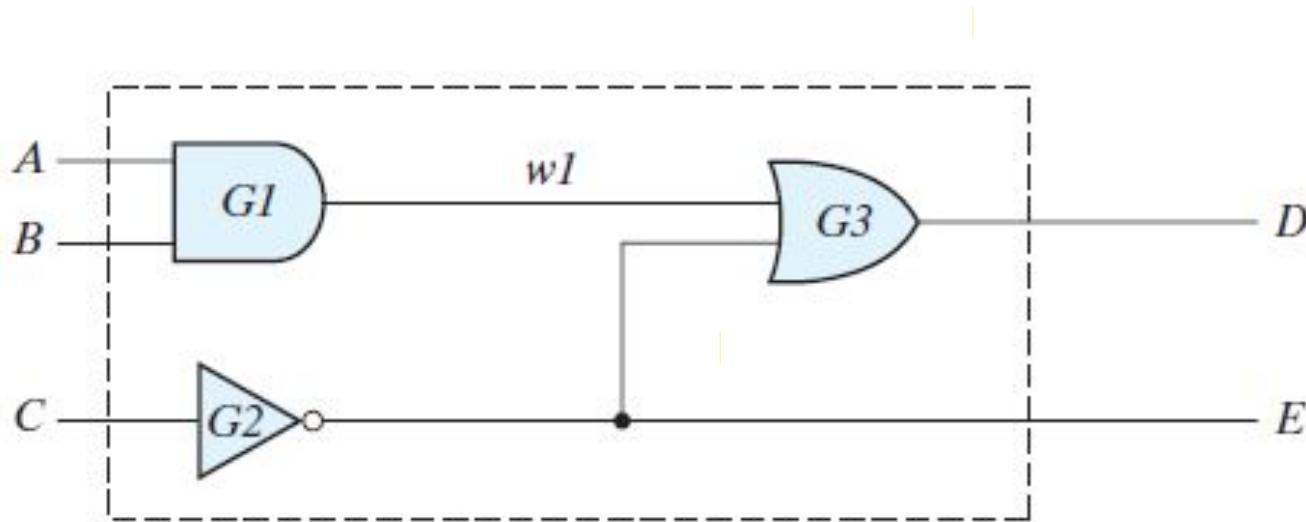
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.


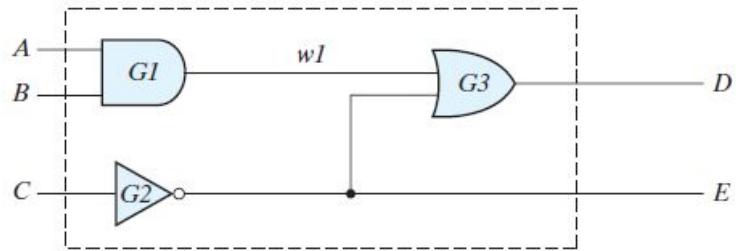
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.




```
module Simple_Circuit (A, B, C, D, E);
```

```
endmodule
```
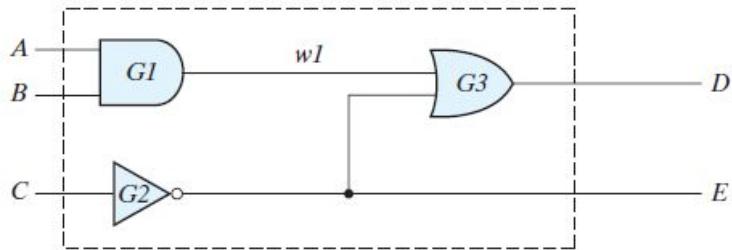
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;

    endmodule
```
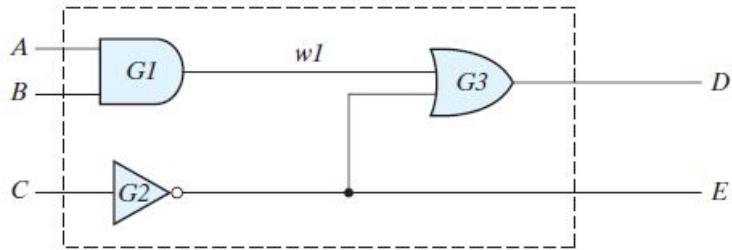
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;

    and G1 (w1, A, B); // Optional gate instance name

    endmodule
```
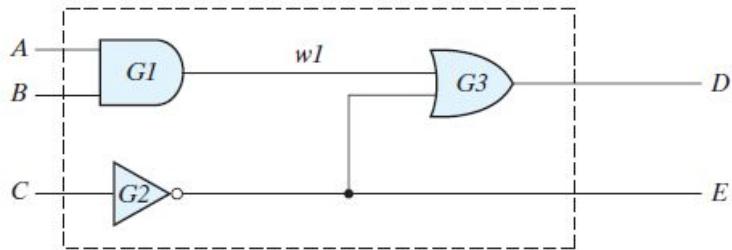
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);

    endmodule
```
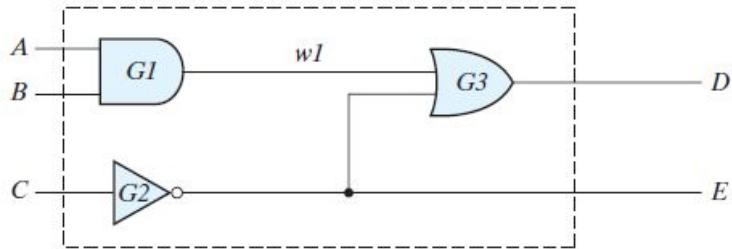
# Short Practice Example 1

Implement a **the circuit given below** using structural design approach.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;

    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);

endmodule
```
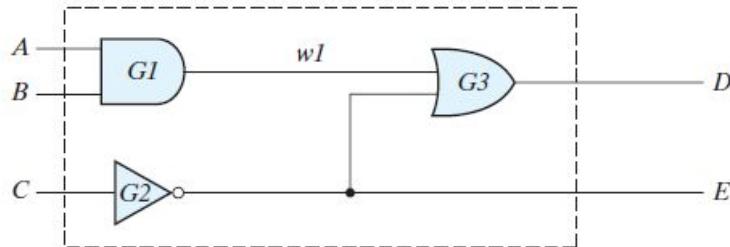
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
```

```
endmodule
```
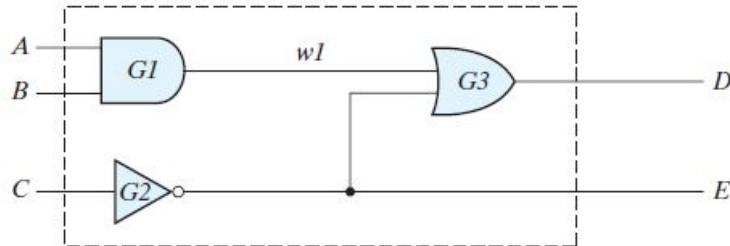
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.



```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and      G1 (w1, A, B); // Optional gate instance name
    not      G2 (E, C);
    or       G3 (D, w1, E);
endmodule
```


```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
    wire D, E;
    reg A, B, C;
```

\*

```
endmodule
```
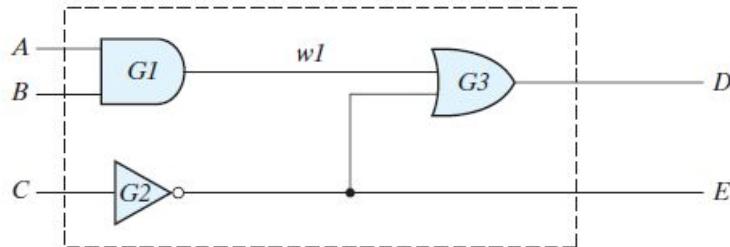
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
    wire D, E;
    reg A, B, C;
    Simple_Circuit M1 (A, B, C, D, E); // Instance name required
endmodule
```
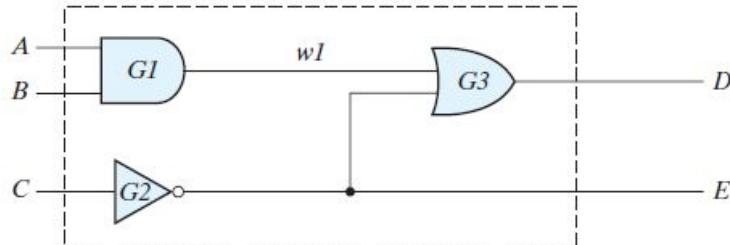
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.




```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
    wire D, E;
    reg A, B, C;
    Simple_Circuit M1 (A, B, C, D, E); // Instance name required
initial
begin
end
endmodule
```
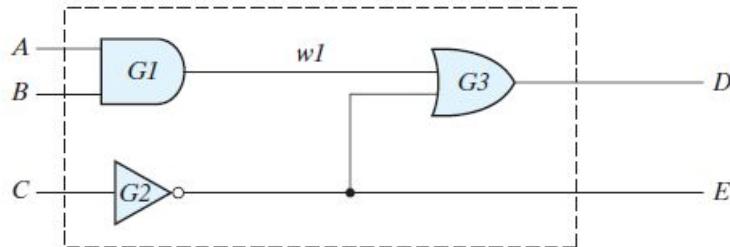
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.



```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;
    and G1 (w1, A, B); // Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
    wire D, E;
    reg A, B, C;


    Simple_Circuit M1 (A, B, C, D, E); // Instance name required

initial
begin
    A = 1'b0; B = 1'b0; C = 1'b0;
    #100 A = 1'b1; B = 1'b1; C = 1'b1;
end

endmodule
```
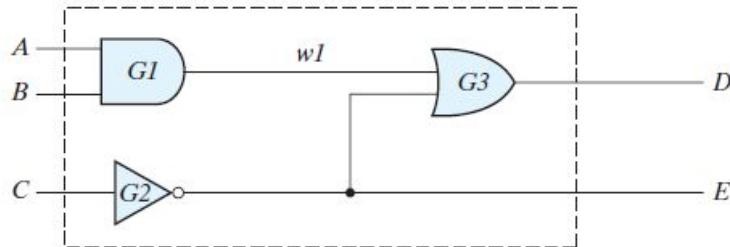
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.



```
module Simple_Circuit (A, B, C, D, E);
  output D, E;
  input A, B, C;
  wire w1;
  and G1 (w1, A, B); // Optional gate instance name
  not G2 (E, C);
  or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
  wire D, E;
  reg A, B, C;


  Simple_Circuit M1 (A, B, C, D, E); // Instance name required

initial
  begin
    A = 1'b0; B = 1'b0; C = 1'b0;
    #100 A = 1'b1; B = 1'b1; C = 1'b1;
  end

  initial #200 $finish;
endmodule
```
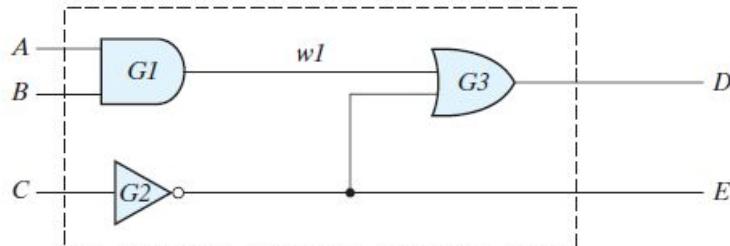
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.



```
module Simple_Circuit (A, B, C, D, E);
  output D, E;
  input A, B, C;
  wire w1;
  and G1 (w1, A, B); // Optional gate instance name
  not G2 (E, C);
  or G3 (D, w1, E);
endmodule
```

```
// Test bench for Simple_Circuit
`include "Simple_Circuit.v"
module t_Simple_Circuit;
  wire D, E;
  reg A, B, C;

  Simple_Circuit M1 (A, B, C, D, E); // Instance name required


  initial
    begin
      A = 1'b0; B = 1'b0; C = 1'b0;
      #100 A = 1'b1; B = 1'b1; C = 1'b1;
    end

  initial #200 $finish;
endmodule
```

Is the delay in ms, ns...?
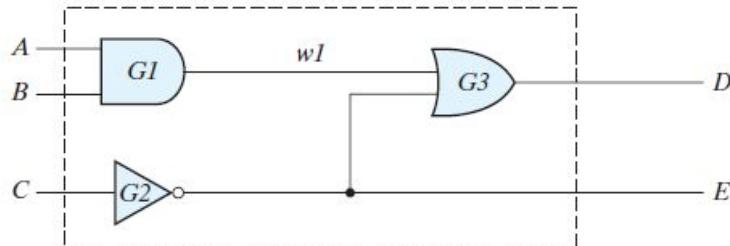
# Short Practice Example 1

Implement a **testbench** for the Simple\_Circuit.



```
module Simple_Circuit (A, B, C, D, E);
  output D, E;
  input A, B, C;
  wire w1;
  and G1 (w1, A, B); // Optional gate instance name
  not G2 (E, C);
  or G3 (D, w1, E);
endmodule
```

```
'timescale 1ns/100ps
`include "Simple_Circuit.v"
module t_Simple_Circuit;
  wire D, E;
  reg A, B, C;

  Simple_Circuit M1 (A, B, C, D, E); // Instance name required

initial
begin
  A = 1'b0; B = 1'b0; C = 1'b0;
  #100 A = 1'b1; B = 1'b1; C = 1'b1;
end

initial #200 $finish;
endmodule
```

You should specify  
the timescale

# Short Practice Example 2

Implement the circuit specified by **the given Boolean equations** using **behavioral** design approach.

$$E = A + BC + B'D$$

$$F = B'C + BC'D'$$

# Short Practice Example 2

Implement the circuit specified by **the given Boolean equations** using **behavioral** design approach.

$$E = A + BC + B'D$$

$$F = B'C + BC'D'$$

```
// Verilog model: Circuit with Boolean expressions
module Circuit_Boolean_CA (E, F, A, B, C, D);
    // Verilog code for the circuit implementation
endmodule
```

# Short Practice Example 2

Implement the circuit specified by **the given Boolean equations** using **behavioral** design approach.

$$E = A + BC + B'D$$

$$F = B'C + BC'D'$$

```
// Verilog model: Circuit with Boolean expressions
module Circuit_Boolean_CA (E, F, A, B, C, D);
    output      E, F;
    input       A, B, C, D;

endmodule
```

# Short Practice Example 2

Implement the circuit specified by **the given Boolean equations** using **behavioral** design approach.

$$E = A + BC + B'D$$

$$F = B'C + BC'D'$$

```
// Verilog model: Circuit with Boolean expressions
module Circuit_Boolean_CA (E, F, A, B, C, D);
    output      E, F;
    input       A, B, C, D;

    assign E = A || (B && C) || ((!B) && D);
    assign F = ((!B) && C) || (B && (!C) && (!D));
endmodule
```

# Short Practice Example 2

Implement the circuit specified by **the given Boolean equations** using **behavioral** design approach.

$$\begin{aligned}E &= A + BC + B'D \\F &= B'C + BC'D'\end{aligned}$$

```
// Verilog model: Circuit with Boolean expressions  
  
module Circuit_Boolean_CA (E, F, A, B, C, D);  
    output E, F;  
    input A, B, C, D;  
  
    assign E = A || (B && C) || ((!B) && D);  
    assign F = ((!B) && C) || (B && (!C) && (!D));  
endmodule
```


Think about how a  
**TESTBENCH** would look like

# Questions?

# Lab Example

Implement a **4-Bit Ripple Carry Adder** in Verilog in the following steps:

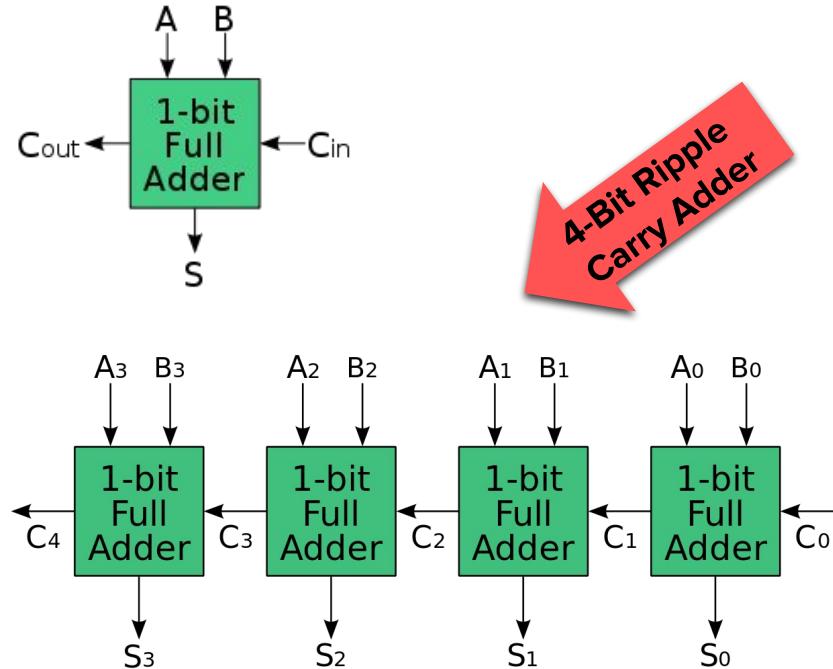
1. Implement a **1-Bit Full Adder** using behavioral design approach. Fill in the truth table, find the corresponding functions for *Sum* and *Carry\_out*, write a Verilog module, test it by writing a testbench for all possible cases.
2. Implement a **4-Bit Ripple Carry Adder** by instantiating your 1-Bit Full Adder module as many times as necessary. Use structural design approach and explicit association. Test it by writing an appropriate testbench.



# Lab Example Solution:


A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
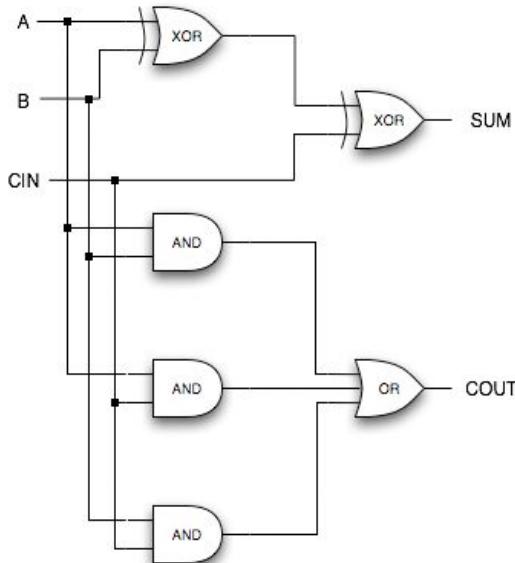
$$\text{sum} = (A \wedge B) \wedge C$$
$$Cout = AB + BC + AC$$



## Full\_Adder.v module

```
module Full_Adder(  
    input A,  
    input B,  
    input Cin,  
    output S,  
    output Cout  
);  
    assign S = (A^B)^Cin;  
    assign Cout = (A&B)|(B&Cin)|(Cin&A);  
endmodule
```

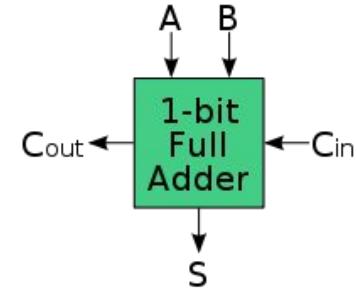

Note the behavioral description

## Full\_Adder\_Testbench.v module

```
module Full_Adder_Testbench;
  //inputs
  reg A, B, Cin;
  //outputs
  wire S, Cout;
  // Instantiate the Unit Under Test (UUT)
  Full_Adder UUT(.A(A), .B(B), .Cin(Cin), .S(S), .Cout(Cout));
  //Provide stimulus
  initial begin
    // Initialize Inputs
    A = 0; B = 0; Cin = 0;
    #10 A = 0; B = 0; Cin = 1;
    #10 A = 0; B = 1; Cin = 0;
    #10 A = 0; B = 1; Cin = 1;
    #10 A = 1; B = 0; Cin = 0;
    #10 A = 1; B = 0; Cin = 1;
    #10 A = 1; B = 1; Cin = 0;
    #10 A = 1; B = 1; Cin = 1;
    #10 $finish;
  end


```

## Simulation results:


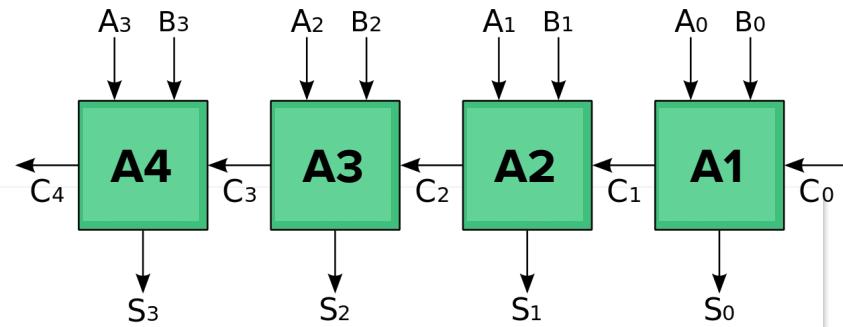
## Four\_Bit\_RCA.v module

```
`include "Full_Adder.v"
module Four_Bit_RCA(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output [3:0] S,
    output Cout
);
    wire [2:0] Carries;
    Full_Adder A1(.A(A[0]),.B(B[0]),.Cin(Cin),.S(S[0]),.Cout(Carries[0]));
    Full_Adder A2(.A(A[1]),.B(B[1]),.Cin(Carries[0]),.S(S[1]),.Cout(Carries[1]));
    Full_Adder A3(.A(A[2]),.B(B[2]),.Cin(Carries[1]),.S(S[2]),.Cout(Carries[2]));
    Full_Adder A4(.A(A[3]),.B(B[3]),.Cin(Carries[2]),.S(S[3]),.Cout(Cout));
endmodule
```



Note the structural  
description and  
explicit association

## Four\_Bit\_RCA\_Testbench.v module

```
module Four_Bit_RCA_Testbench;
    //inputs
    reg [3:0] A, B;
    reg Cin;
    //outputs
    wire [3:0] S;
    wire Cout;
    // Instantiate the Unit Under Test (UUT)
    Four_Bit_RCA UUT(.A(A), .B(B), .Cin(Cin), .S(S), .Cout(Cout));
    //Provide stimulus
    initial begin
        // Initialize Inputs
        A = 4'b0000; B = 4'b0000; Cin = 0;
        #10 A = 4'b0000; B = 4'b0000; Cin = 1;
        #10 A = 4'b1100; B = 4'b0011; Cin = 0;
        #10 A = 4'b1100; B = 4'b0011; Cin = 1;
        #10 A = 4'b1110; B = 4'b0001; Cin = 1;
        #10 A = 4'b1100; B = 4'b0011; Cin = 1;
        #10 A = 4'b1111; B = 4'b0001; Cin = 0;
        #10 A = 4'b1111; B = 4'b1111; Cin = 1;
        #10 $finish;
    end
```

Only some test cases.  
Why not all?

How can we automate  
the process?

# Lab Example 2 - Sequential Circuits

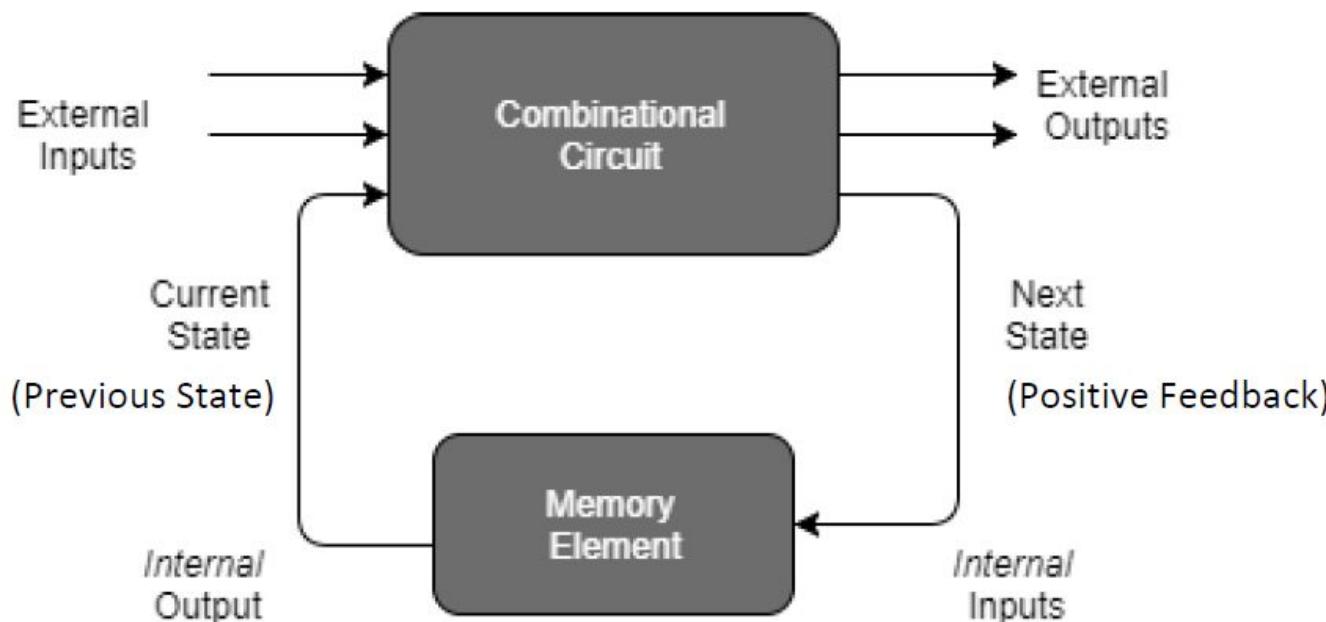


Figure: Sequential Circuit

# Lab Example 2 - Sequential Circuits

Storage Elements

Latches: level-sensitive



Flip-flops: edge-sensitive




Positive-edge response



Negative-edge response
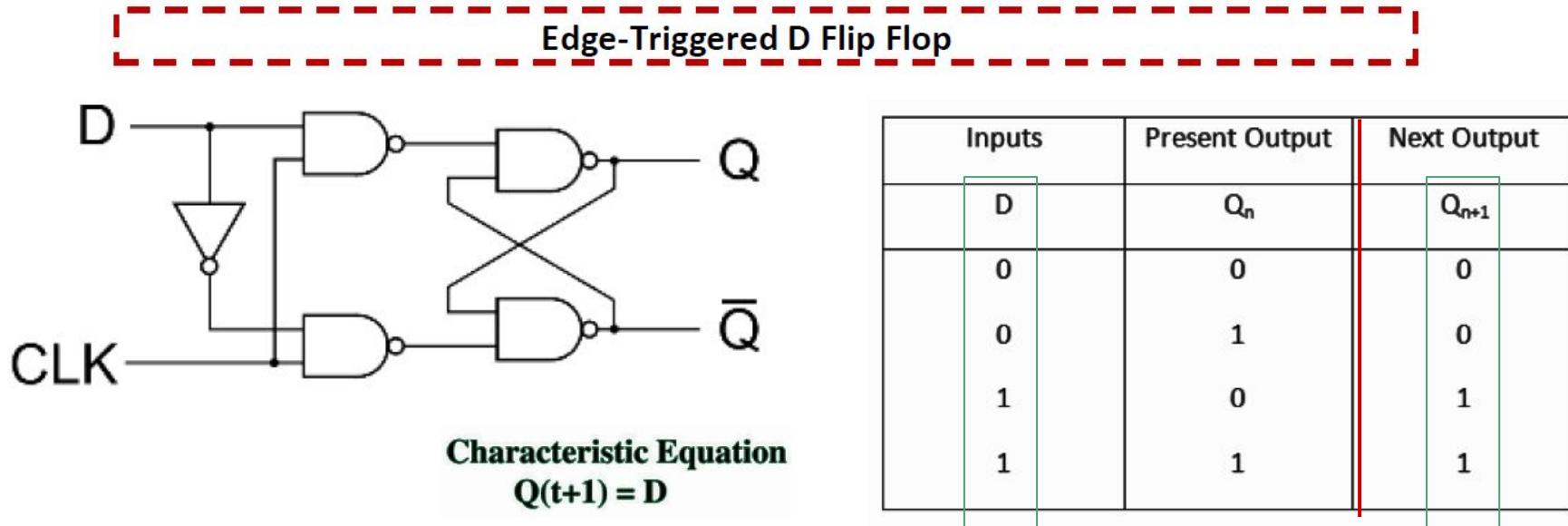
# Lab Example 2 - Sequential Circuits

A flip flop is a basic building block of sequential logic circuits. It is a circuit that has two stable states and can store one bit of state information. The output changes state by signals applied to one or more control inputs.



A basic D Flip Flop has a D (data) input, a clock (CLK) input and outputs Q and Q' (the inverse of Q). Optionally it may also include the PR (Preset) and CLR (Clear) control inputs.

# Lab Example 2 - Sequential Circuits

Verilog codes for different implementations of D flip-flop:

Verilog code for Rising Edge D Flip Flop:

```
module RisingEdge_DFlipFlop(D,clk,Q);
    input D; // Data input
    input clk; // clock input
    output reg Q; // output Q
    always @ (posedge clk)
    begin
        Q <= D;
    end
endmodule
```

Verilog code for Falling Edge D Flip Flop:

```
module FallingEdge_DFlipFlop(D,clk,Q);
    input D; // Data input
    input clk; // clock input
    output reg Q; // output Q
    always @ (negedge clk)
    begin
        Q <= D;
    end
endmodule
```

# Lab Example 2 - Sequential Circuits

Verilog codes for different implementations of D flip-flop:

Verilog code for Rising Edge D Flip Flop with Synchronous Reset:

```
module RisingEdge_DFlipFlop_SyncReset (D, clk, sync_reset, Q);
    input D; // Data input
    input clk; // clock input
    input sync_reset; // synchronous reset
    output reg Q; // output Q
    always @ (posedge clk)
    begin
        if (sync_reset==1'b1)
            Q <= 1'b0;
        else
            Q <= D;
    end
endmodule
```

# Lab Example 2 - Sequential Circuits

## Sequential Circuit Design (With an Example)

Here we state the steps of designing a sequential circuit with an example circuit specification:

### 111 Sequence Detector:


Design a circuit that outputs 1 when a sequence three consecutive 1's is applied to input, and 0 otherwise.

<b>Input</b>	X	0 1 1 1 0 0 0 1 1 1 1 1 0 0 0
<b>Output</b>	Y	0 0 0 1 0 0 0 0 0 1 1 1 0 0 0
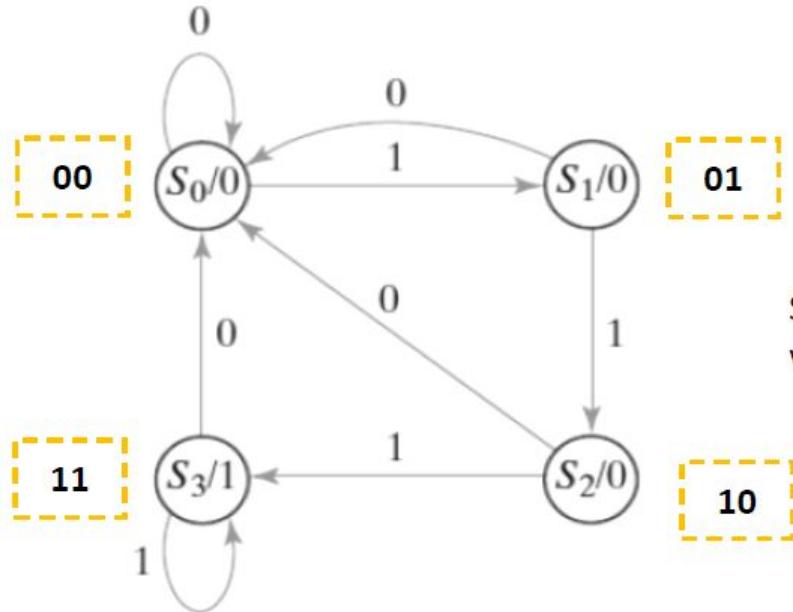
# Lab Example 2 - Sequential Circuits

To design a sequential circuit, start with the problem definition and use the following steps:


- Step-1: Create a state transition diagram from the description. Reduce the number of states if necessary, and assign binary values to the states.



State diagram for 111 Sequence Detector with assigned binary values to the states.
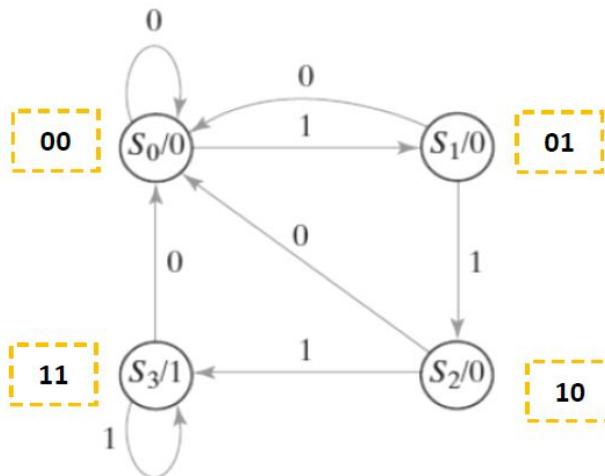
# Lab Example 2 - Sequential Circuits

- Step-2: Convert the state transition diagram into a state transition table (binary coded state table).



*State Table for Sequence Detector*

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<b>A</b>	<b>B</b>		<b>A</b>	<b>B</b>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

# Lab Example 2 - Sequential Circuits

- Step-3: Determine the number of flip-flops needed and choose flip-flop types. Derive their excitation tables (if designing a sequential circuit with flip-flops other than the D type), and derive input and output equations from the state table. Minimize the functions for the flip-flop inputs (e.g. using Karnaugh Maps).

We choose D-type flip-flops. Since there are four states, we need two D flip-flops, and we label their outputs as A and B. The characteristic equation of the D flip-flop is  $Q(t + 1) = D$ , which means that the next-state values in the state table specify the D input condition for the flip-flop.

# Lab Example 2 - Sequential Circuits


*State Table for Sequence Detector*

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

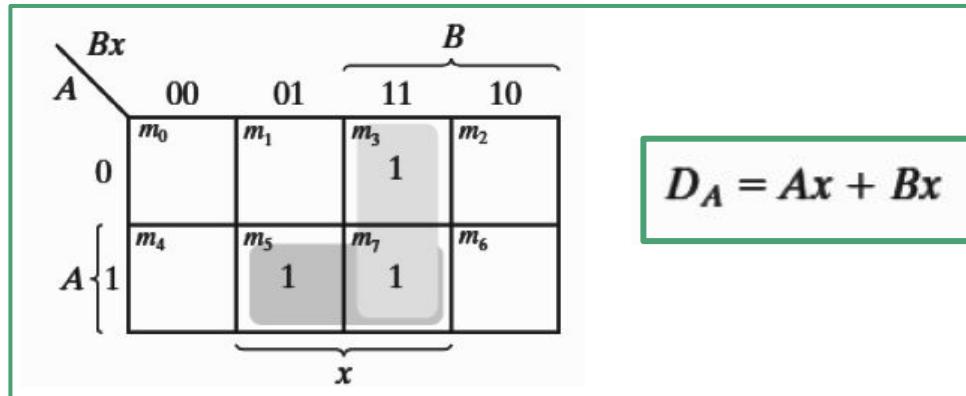
**Characteristic Equation**  

$$Q(t+1) = D$$


From the state table above we obtain the following input equations:



$$D_A = Ax + Bx$$

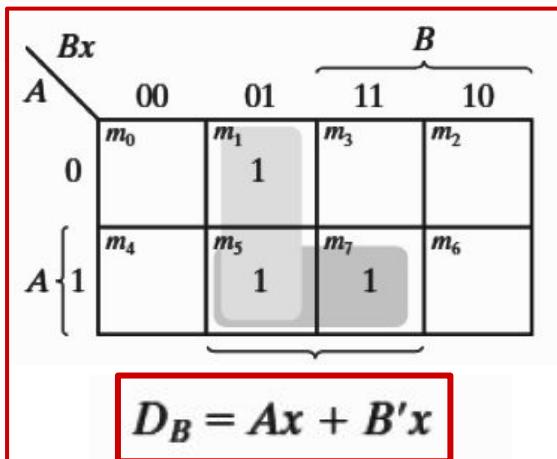


$$D_B = Ax + B'x$$

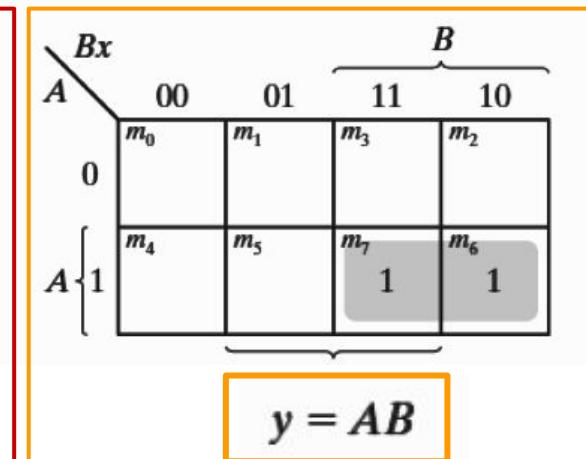

$$y = AB$$
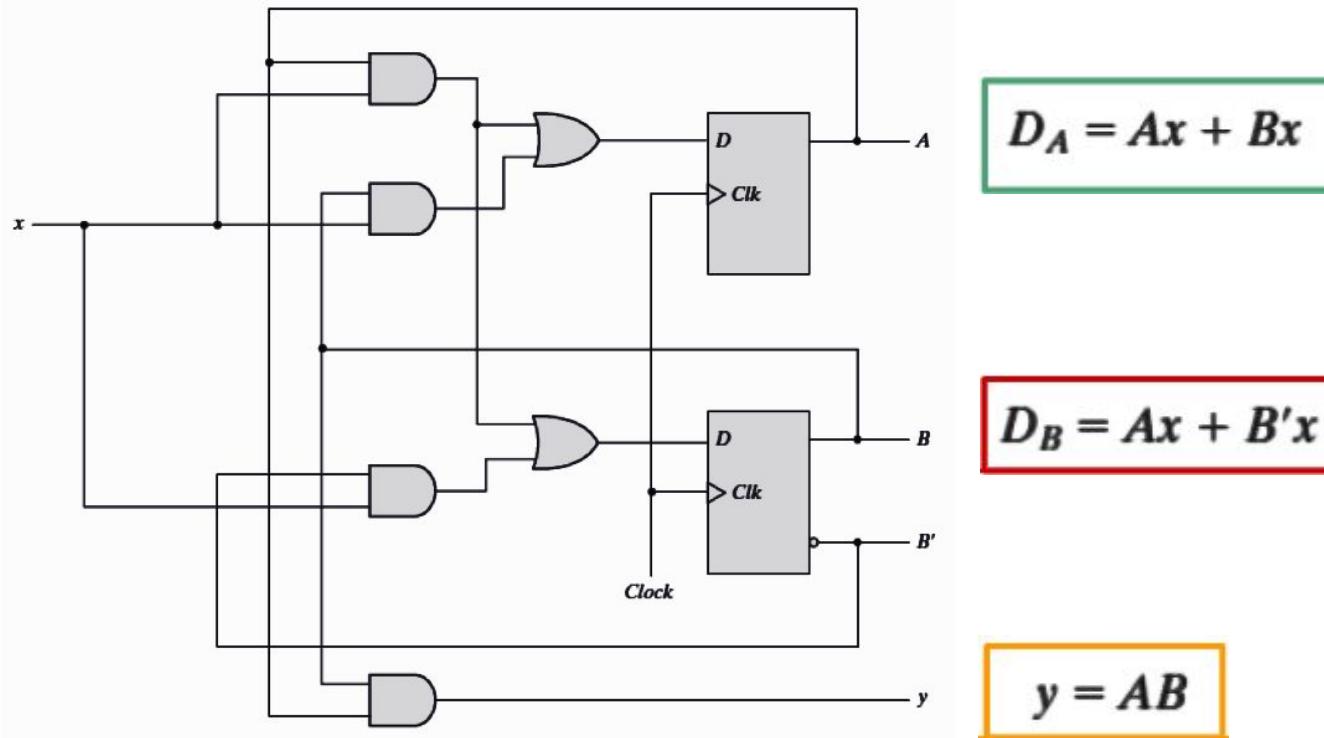
# Lab Example 2 - Sequential Circuits

- Step-4: Use simplified functions for D1 and D2 to design sequential circuit.
- Step-5: Finally determine the combinatorial circuit to represent the output (if any).



# Lab Example 2 - Sequential Circuits

Verilog Code for the 111 Sequence Detector


Structural design using flip-flops:

```
module D_ff(D, clk, Q); // Rising-edge D flip flop
    input D; // Data input
    input clk; // clock input
    output reg Q; // output Q

    always @(posedge clk)
    begin
        Q <= D;
    end
endmodule
```

Let's choose rising-edge  
D flip-flop
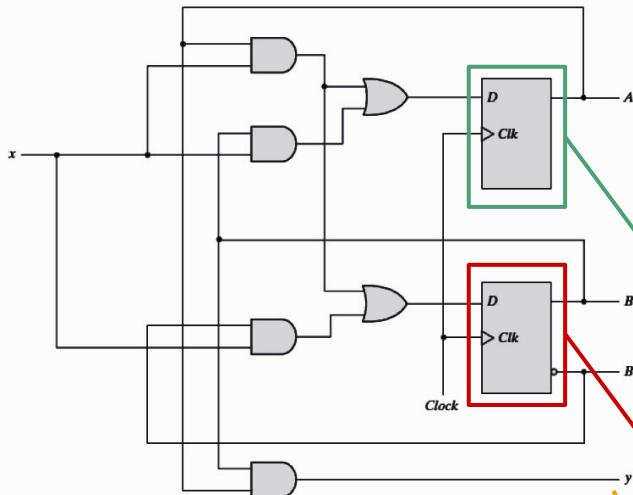
# Verilog Code for the 111 Sequence Detector



```
module D_ff(D, clk, Q); // Rising-edge D flip flop
    input D; // Data input
    input clk; // clock input
    output reg Q; // output Q

    always @(posedge clk)
    begin
        Q <= D;
    end
endmodule
```

Remember the equations:

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

```
'include "D_ff.v"
module three_1s_seq_detector(
    input x_in,
    input clock,
    input reset,
    output y);

reg [1:0] present_state = 2'b00;
wire [1:0] next_state;

D_ff D1 (
    .D((present_state[1]&x_in)|(present_state[0]&x_in)),
    .clk(clock),
    .Q(next_state[1])
);

D_ff D0 (
    .D((present_state[1]&x_in)|(~present_state[0]&x_in)),
    .clk(clock),
    .Q(next_state[0])
);

always @ (reset or next_state) begin
    if (reset) begin present_state <= 2'b00; end
    else begin present_state <= next_state; end
end
assign y = present_state[1] & present_state[0];
endmodule
```

Let's look at the code in parts...

## Verilog Code for the 111 Sequence Detector

```
'include "D_ff.v"

module three_1s_seq_detector(
    input x_in,
    input clock,
    input reset,
    output y);

reg [1:0] present_state = 2'b00;

wire [1:0] next_state;
```

Include D\_ff module

Declare I/O ports

present\_state[1] to store A  
present\_state[0] to store B

next\_state[1] to represent  $D_A$   
next\_state[0] to represent  $D_B$

## Verilog Code for the 111 Sequence Detector

Instantiating D flip flops:

```
D_ff D1 (
    .D((present_state[1]&x_in)|(present_state[0]&x_in)),
    .clk(clock),
    .Q(next_state[1])
);
```

$$D_A = Ax + Bx$$

```
D_ff D0 (
    .D((present_state[1]&x_in)|(~present_state[0]&x_in)),
    .clk(clock),
    .Q(next_state[0])
);
```

$$D_B = Ax + B'x$$

## Verilog Code for the 111 Sequence Detector

Handle reset and update present\_state on change of next\_state:

```
always @(reset or next_state) begin  
    if (reset) begin present_state <= 2'b00; end  
    else begin present_state <= next_state; end  
end
```

Combinational circuit to implement the output:

```
assign y = present_state[1] & present_state[0];
```

How would you make output y implemented  
in structural design approach as well?

$$y = AB$$

# Verilog Code for the 111 Sequence Detector

An alternative behavioral design in Verilog:

```
module three_1s_seq_detector_behavioral(
    input x_in,
    input clock,
    input reset,
    output y);
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
reg [1:0] state, next_state;


always@(posedge clock, negedge reset)
    if (reset == 0) state <= s0;
    else state <= next_state;

always@(state, x_in) begin
    case(state)
        s0: if (x_in == 0) next_state = s0;
            else if (x_in == 1) next_state = s1;
        s1: if (x_in == 0) next_state = s0;
            else if (x_in == 1) next_state = s2;
        s2: if (x_in == 0) next_state = s0;
            else if (x_in == 1) next_state = s3;
        s3: if (x_in == 0) next_state = s0;
            else if (x_in == 1) next_state = s3;
            default: next_state = s0;
    endcase
end
assign y = state[1] & state[0];
endmodule
```

Note different reset implementation

Note multiple always blocks

Solution No. 2 -  
Behavioral design

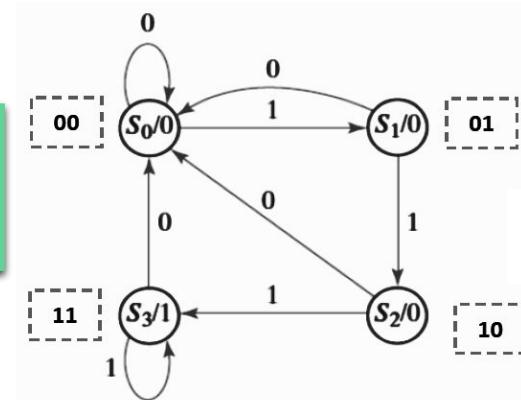

## Verilog Code for the 111 Sequence Detector


An alternative behavioral design in Verilog:

```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
```

```
always@(state, x_in) begin
    case(state)
        s0: if (x_in == 0) next_state = s0;
        else if (x_in == 1) next_state = s1;
        s1: if (x_in == 0) next_state = s0;
        else if (x_in == 1) next_state = s2;
        s2: if (x_in == 0) next_state = s0;
        else if (x_in == 1) next_state = s3;
        s3: if (x_in == 0) next_state = s0;
        else if (x_in == 1) next_state = s3;
        default: next_state = s0;
    endcase
end
```

Whenever input x or state change

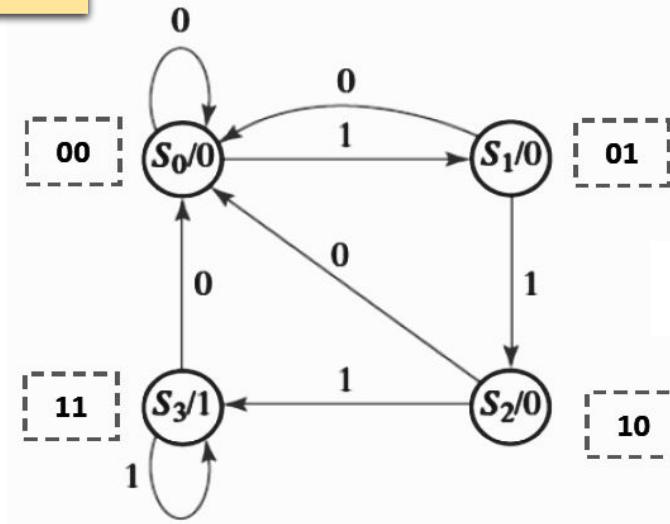Use parameter to give constant names to your states



# Lab Example 2 - Sequential Circuits

**How would we design a testbench for a sequence detector?**

The idea is to have an input bit stream (e.g. a 20-bit binary sequence),

```
input_data = 20'b0000111010011100000;
```

and send one input bit at a time at each clock cycle (e.g. using shifting).

```
always @ (posedge clk) begin
    x = input_data>>shift_amount; // get the next input bit
    shift_amount=shift_amount+1;
end
```

## Entire sample testbench code:

```
module three_ls_seq_detector_tb;
    // Inputs
    reg x;
    reg clk;
    reg rst;
    // Outputs
    wire y;
    // Instantiate the Unit Under Test (UUT)
    three_ls_seq_detector uut (.x_in(x), .clock(clk), .reset(rst), .y(y));
    reg [19:0] input_data;
    integer shift_amount;
    initial begin
        // Initialize Inputs
        input_data = 20'b00001110100111100000;
        shift_amount=0;
        rst = 1; #50;
        rst = 0; #500; $finish;
    end
    initial begin // Generate clock
        clk = 0;
        forever begin
            #10;
            clk = ~clk; // change every 10ns
        end
    end
    always @ (posedge clk) begin
        x = input_data>>shift_amount; // get the next input bit
        shift_amount=shift_amount+1;
    end
endmodule
```

# References

- Slides are mostly based on: NPTEL Online Certification Course on Hardware Modeling Using Verilog, by Prof. Indranil Sengupta, Department of Computer Science and Engineering, Indian Institute of Technology Kharagpur - Available online at:  
<https://www.youtube.com/playlist?list=PLUtfVcb-iqn-EkuBs3arreilxa2UKIChl>
- Digital Design, M. Morris Mano and Michael D. Ciletti, Prentice Hall.
- Verilog for Sequential Circuits, Design of Digital Circuits 2014, Srdjan Capkun, Frank K. Gürkaynak. Available online at:  
[https://syssec.ethz.ch/content/dam/ethz/special-interest/infk/inst-infsec/system-security-group-dam/education/Digitaltechnik\\_14/09\\_Verilog\\_Sequential.pdf](https://syssec.ethz.ch/content/dam/ethz/special-interest/infk/inst-infsec/system-security-group-dam/education/Digitaltechnik_14/09_Verilog_Sequential.pdf)
- Digital VLSI Systems Design, A Design Manual for Implementation of Projects on FPGAs and ASICs Using Verilog, Dr. Seetharaman Ramachandran, Springer.