

Verilog Tutorial-2

COMBINATIONAL CIRCUIT

Vector

- Nets or “reg” type variable can be declared as vectors, of multiple bit widths.
 - If bit width is not specified, default size is 1-bit.
- Vectors are declared by specifying a range [range1:range2], where range1 is always the most significant bit and range2 is the least significant bit.
- Examples:

wire x, y, z; // Single bit variables

wire [7:0] sum; // MSB is sum[7], LSB is sum[0]

reg [31:0] MDR;

8 bit adder

```
// An 8-bit adder description  
module paralle_adder (sum, cout, in1, in2, cin);  
    input [7:0] in1, in2; input cin;  
    output [7:0] sum;  
    output cout;  
    assign #20 {cout,sum} = in1 + in2 + cin;  
endmodule
```

Test bench

```
module tb_8bit Adder;

    reg [7:0] A, B;

    reg C;

    wire [7:0] SUM;

    wire Cr;

    adder8bit fa8 (.sum( SUM), .cr( Cr),.a( A), .b( B), .c( C));

    initial

    begin

        $dumpfile ("8bitadder.vcd");

        $dumpvars (0,8bitadder);

        $monitor (" $time A=%d B=%d C=%c SUM=%d Cr=%d", A, B, C, SUM, Cr);

        #0 A=4'b0000; B=4'b0000; C=1'b0;

        #10 A=4'b0100; B=4'b0011; C=1'b1;

        #20 A=4'b0011; B=4'b0111; C=1'b1;

        #30 A=4'b1000; B=4'b0100; C=1'b0;

        #40 A=4'b0101; B=4'b0101; C=1'b1;

    end

endmodule
```

2 bit comparator

```
// A 2-bit comparator
module compare (A1, A0, B1, B0, lt, gt, eq);
input A1, A0, B1, B0;
output reg lt, gt, eq;
always @ (A1, A0, B1, B0)
begin
    lt = ({A1,A0} < {B1,B0});
    gt = ({A1,A0} > {B1,B0});
    eq = ({A1,A0} == {B1,B0});
end
endmodule
```

N-bit comparator

```
// An n-bit comparator
module compare (A, B, lt, gt, eq);
    parameter word_size = 16;
    input [word_size-1:0] A, B;
    output reg lt, gt, eq;

    always @ (*)
    begin
        gt = 0;
        lt = 0; eq = 0;
        if (A > B) gt = 1;
        else if (A < B) lt = 1;
        else eq = 1;
    end
endmodule
```

ALU

```
// A simple 4-function ALU
module ALU_4bit (f, a, b, op);
    input [1:0] op;
    input [7:0] a, b;
    output reg [7:0] f;
    parameter ADD=2'b00, SUB=2'b01, MUL=2'b10, DIV=2'b11;
    always @(*)
        case (op)
            ADD : f = a + b;
            SUB : f = a - b;
            MUL : f = a * b;
            DIV : f = a / b;
        endcase
endmodule
```

Multiplexer

```
module mux16to1 (in, sel, out);  
    input [15:0] in;  
    input [3:0] sel;  
    output out;  
    assign out = in[sel];  
endmodule
```


Test bench for mux

```
module muxtest;

reg [15:0] A; reg [3:0] S; wire F;

mux16to1 M (.in(A), .sel(S), .out(F));

initial

begin

    $dumpfile ("mux16to1.vcd");

    $dumpvars (0,muxtest);

    $monitor ($time," A=%h, S=%h, F=%b", A,S,F);

    #5 A=16'h3f0a; S=4'h0;

    #5 S=4'h1;

    #5 S=4'h6;

    #5 S=4'hc;

    #5 $finish;

end

endmodule
```

0	A=xxxx,	S=x,	F=x
5	A=3f0a,	S=0,	F=0
10	A=3f0a,	S=1,	F=1
15	A=3f0a,	S=6,	F=0
20	A=3f0a,	S=c,	F=1

Another kind of behavioural modelling

// A combinational logic example

```
module mux21 (in1, in0, s, f);
```

```
  input in1, in0, s;
```

```
  output reg f;
```

```
  always @(*)
```

```
    if (s)
```


```
      f = in1;
```

```
    else
```

```
      f = in0;
```

```
endmodule
```

If we want to do structural modelling

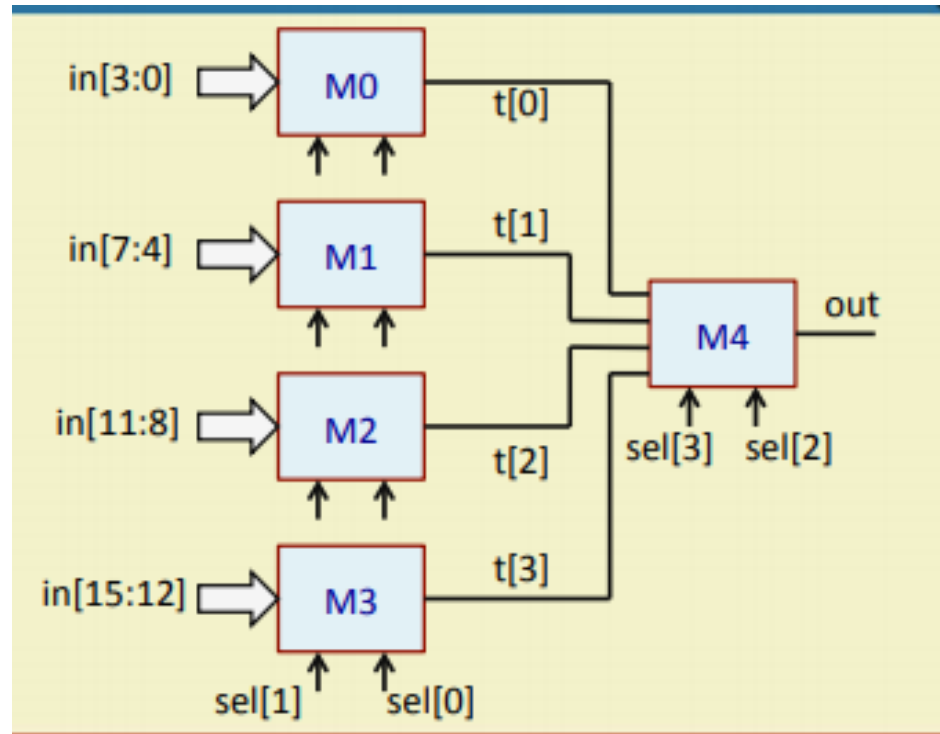

To make a structural modelling of large circuit we use the technique of hierarchical model and break down in such a way that the simplest form is easy to model structurally.


16x1 using 4x1 mux

```
module mux4to1 (in, sel, out);  
    input [3:0] in;  
    input [1:0] sel;  
    output out;  
    assign out = in[sel];  
endmodule
```

```
module mux16to1 (in, sel, out);  
    input [15:0] in;  
    input [3:0] sel;  
    output out;  
    wire [3:0] t;  
    mux4to1 M0 (in[3:0],sel[1:0],t[0]);  
    mux4to1 M1 (in[7:4],sel[1:0],t[1]);  
    mux4to1 M2 (in[11:8],sel[1:0],t[2]);  
    mux4to1 M3 (in[15:12],sel[1:0],t[3]);  
    mux4to1 M4 (t,sel[3:2],out);  
endmodule
```

4x1 mux using 2x1 mux
 
```
module mux2to1 (in, sel, out);  
    input [1:0] in;  
    input sel; output out;  
    assign out = in[sel];  
endmodule
```



```
module mux4to1 (in, sel, out);  
    input [3:0] in;  
    input [1:0] sel;  
    output out;  
    wire [1:0] t;  
    mux2to1 M0 (in[1:0],sel[0],t[0]);  
    mux2to1 M1 (in[3:2],sel[0],t[1]);  
    mux2to1 M2 (t,sel[1],out);  
endmodule
```

Simplest module (2x1 mux)

```
module mux2to1 (in, sel, out);  
  input [1:0] in; input sel;  
  output out;  
  wire t1, t2, t3;  
  NOT G1 (t1,sel);  
  AND G2 (t2,in[0],t1);  
  AND G3 (t3,in[1],sel);  
  OR G4 (out,t2,t3);  
endmodule
```

Simple decoder (try to build larger decoder)

```
module generate_decoder (out, in, select);  
    input in;  
    input [0:1] select;  
    output [0:3] out;  
    assign out[select] = in;  
endmodule
```

Thank You
